

**BASIC ELECTRONICS LAB**  
**EC29201**  
**LAB REPORT**  
**BATCH 5**


Experiment No. : 2 (Ohm's Law and RC Circuits(Filters and rectifiers))

Report By: Swarup Padhi  
Roll No.:20CS30062

# Part-1

**AIM** : To Verify Ohm's Laws in Resistors, Series Combinations, Parallel Combinations and explain working principle of Non Ohmic Devices

# Ohm's Law (Circuit Diagram):

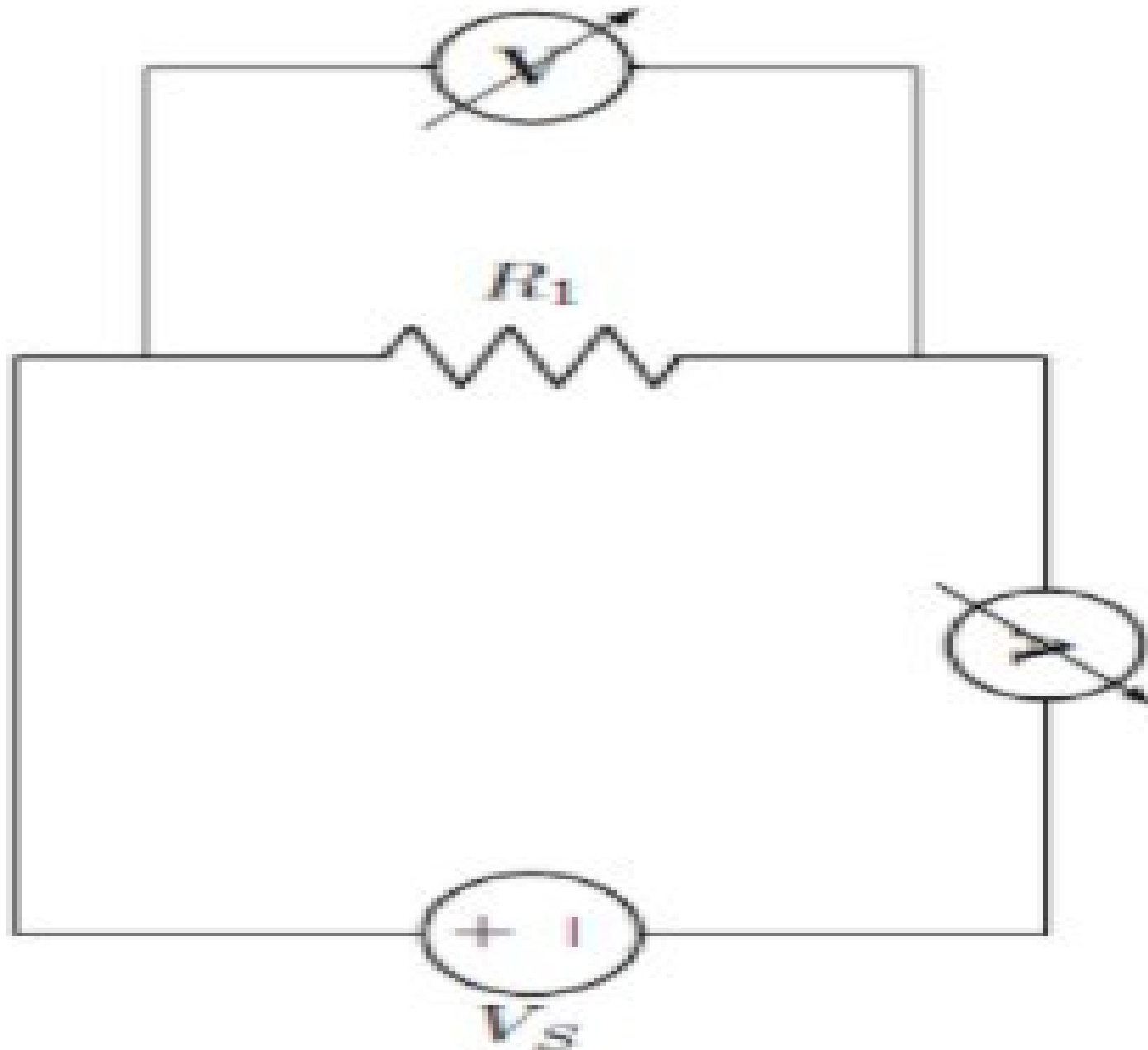

## Ohm's Law (theory):

Ohm's law states that the current flowing in a resistor is directly proportional to the applied potential difference and inversely proportional to the resistance in the circuit

If  $I$  is the current flowing through a conducting wire and  $V$  is the potential difference across the ends of the conducting wire, then according to Ohm's law (At constant temperature):

$$\Rightarrow I \propto V$$

Such a conductor is characterized by its 'Resistance' -  $R$  measured in Ohms.

$V = I * R$  where  $V$  is voltage in volts,  $I$  is current in amperes and  $R$  is resistance in ohms

# Ohm's Law (simulated data):

## INSTRUCTION

### EXPERIMENTAL TABLE


Resistance( $R_1$ ): 75 K $\Omega$

Resistance( $R_2$ ): 10 K $\Omega$

Resistance( $R_{eq}$ ): 85 K $\Omega$

Serial No.	Voltage(Volt) V	Current(milliAmpere) mA
1	5	0.0588
2	10	0.118
3	12	0.141
4	15	0.176
5	20	0.235
6	25	0.294

## Ohm's Law Series

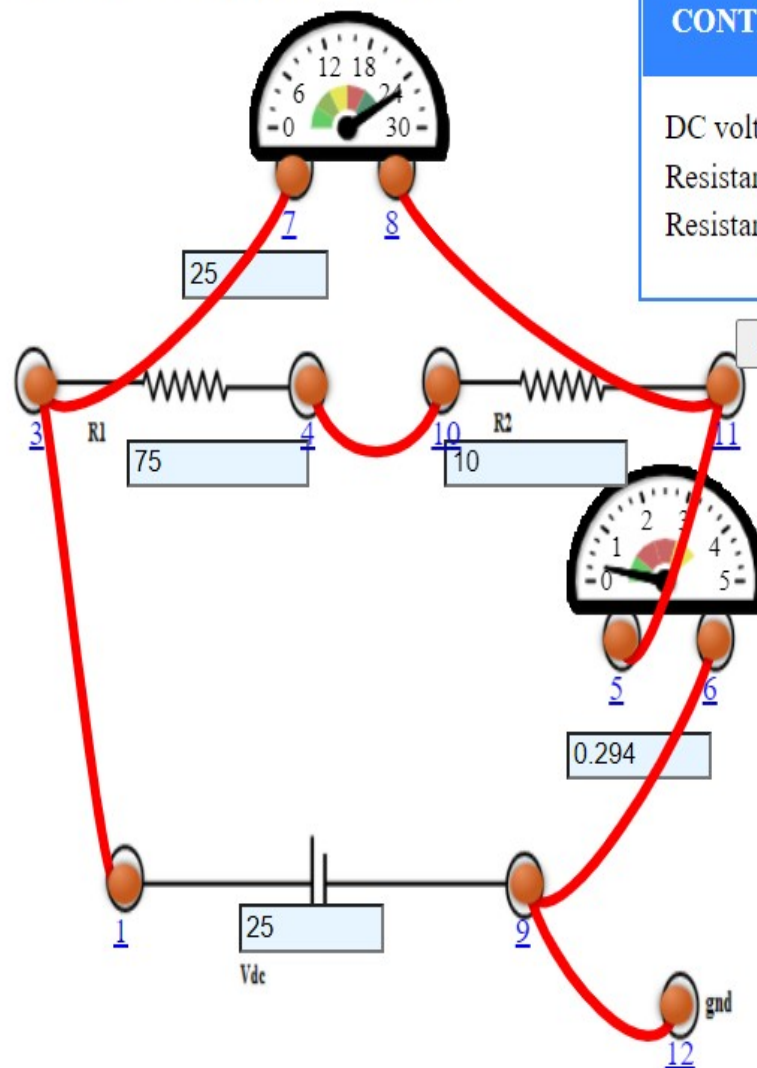

### CONTROLS

DC volt :  Volt  
Resistance1 :  Kohms  
Resistance2 :  Kohms

Add to Table

Plot

Clear


Check  
connection

Delete all  
connection

Print It

Take another sets of Voltmeter and  
Ammeter readings for another Resistance  
value

# Ohm's Law (Graph):

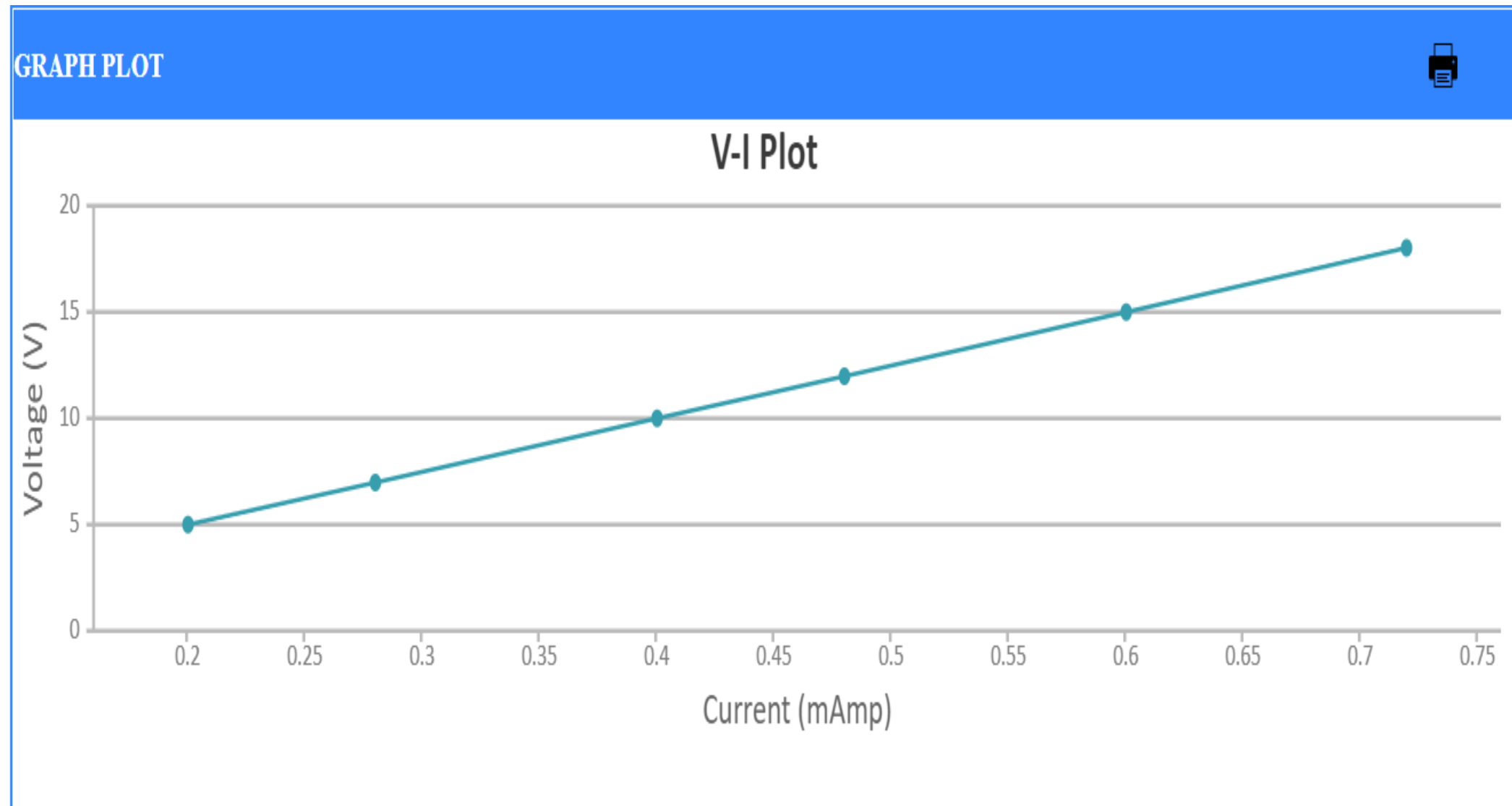

## Ohm's Law for Resistance in series (Circuit Diagram):

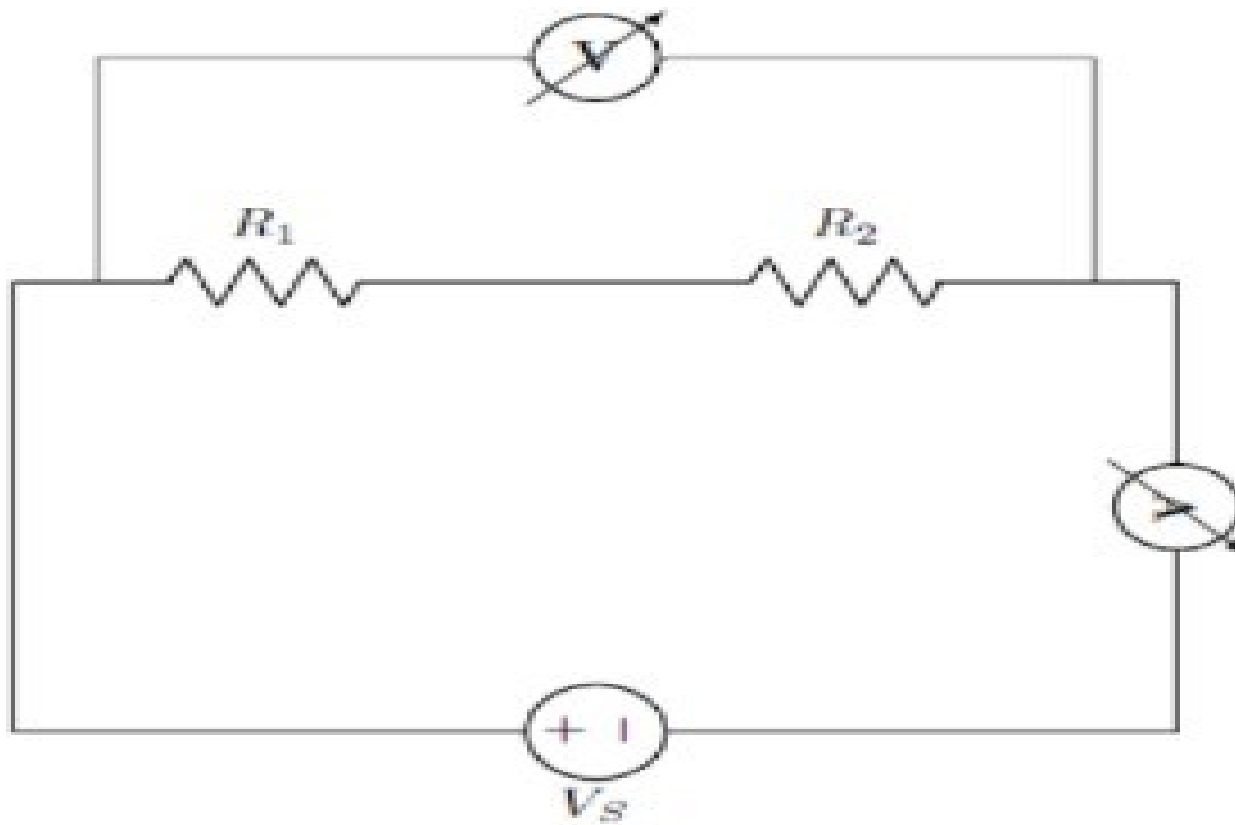


Figure 3: Series resistors

# Ohm's Law for Resistance in Series(Theory)

According to Ohm's law,  $V=I*R$ , and in series connection of resistances same current flows to each resistor  $R_1$  and  $R_2$ , So the voltage drop across  $R_1$  is  $V_1=I*R_1$  and across  $R_2$  is  $V_2=I*R_2$

If we substitute the values for individual voltages, we get:  
 $V_T=I_T*(R_1+R_2)$

This gives the equivalent resistance as

$$R_{eq}=R_1 + R_2$$

$$I_T = V_T / R_{eq}$$



# Ohm's Law for Resistances in Series (Simulated Data)


## INSTRUCTION

## EXPERIMENTAL TABLE

Resistance( $R_1$ ): 75 K $\Omega$   
Resistance( $R_2$ ): 10 K $\Omega$   
Resistance( $R_{eq}$ ): 85 K $\Omega$

Serial No.	Voltage(Volt) V	Current(milliAmpere) mA
1	5	0.0588
2	10	0.118
3	12	0.141
4	15	0.176
5	20	0.235
6	25	0.294

## Ohm's Law Series

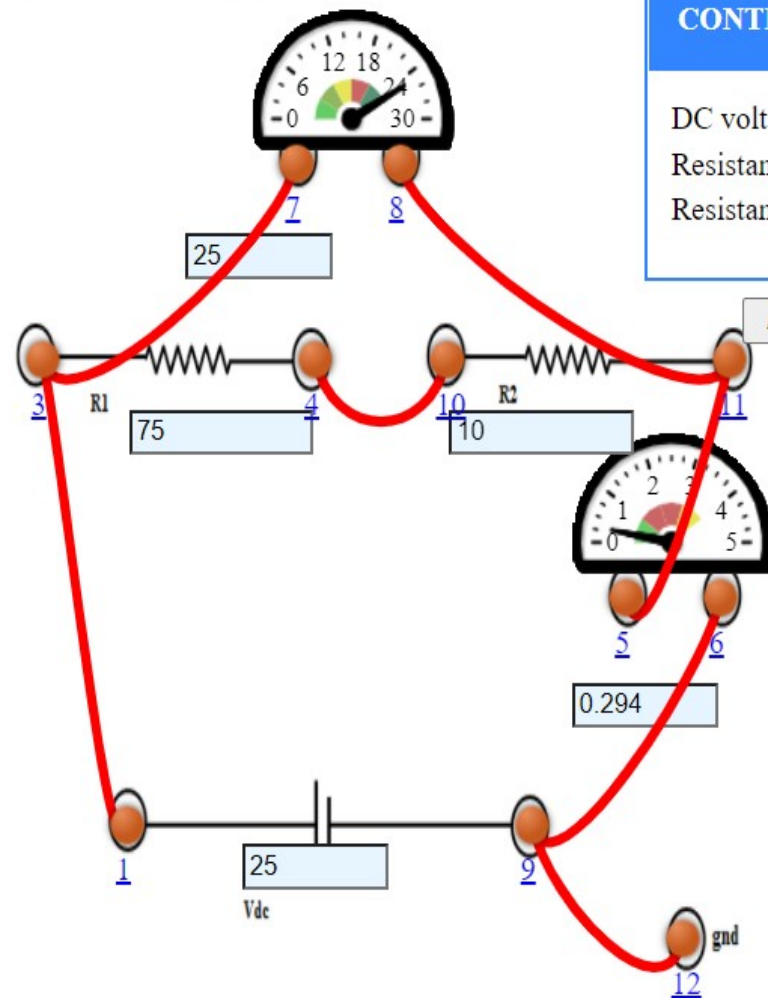

## CONTROLS

DC volt :  Volt  
Resistance1 :  Kohms  
Resistance2 :  Kohms

Add to Table

Plot

Clear

Check  
connection

Delete all  
connection

Print It


Take another sets of Voltmeter and  
Ammeter readings for another Resistance  
value

# Ohm's Law for Resistances in series(Graph)

GRAPH PLOT



V-I Plot

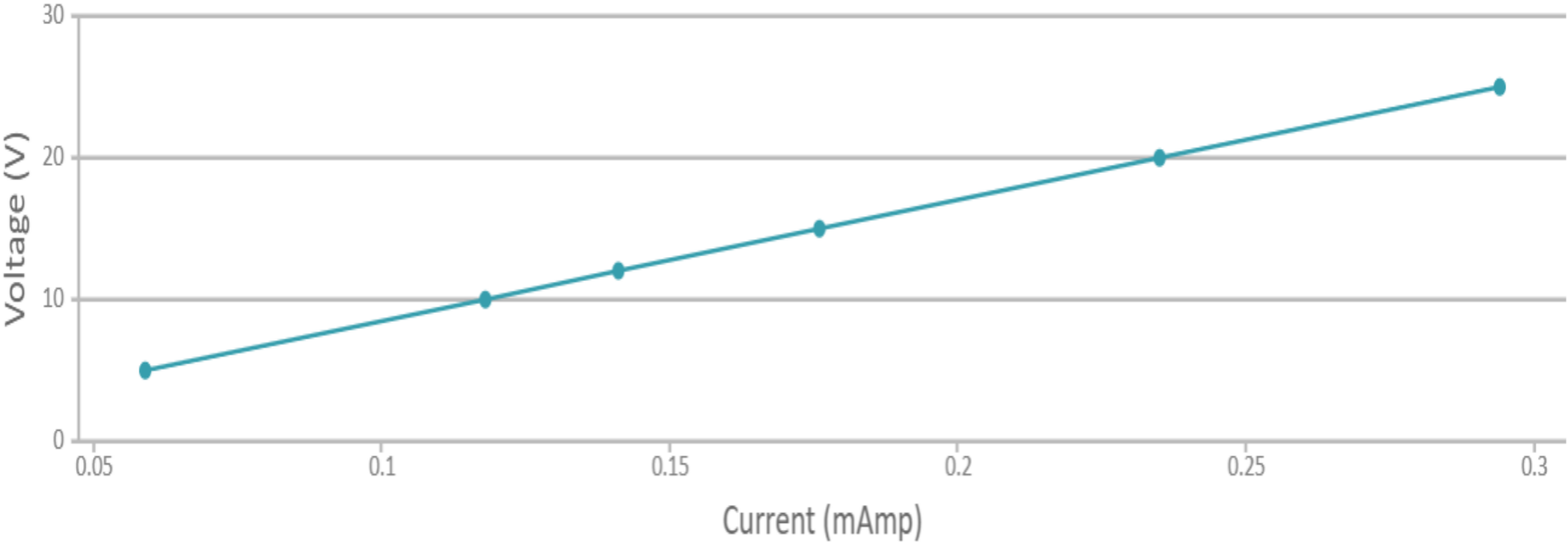

## Ohm's Law for Resistance in Parallel(Circuit Diagram) :

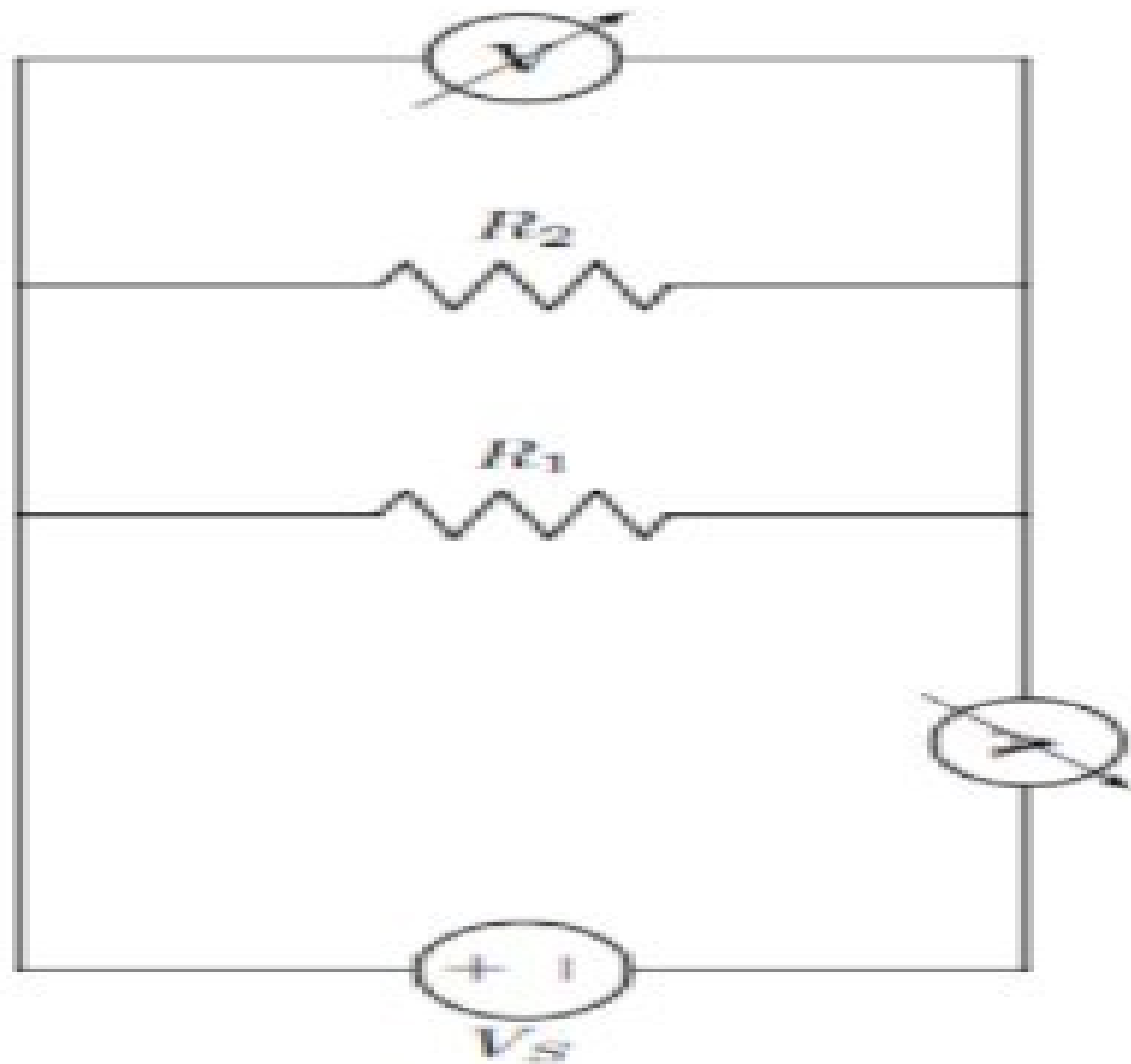


Figure 4: Parallel resistors

# Ohm's Law for Resistance in Parallel (Theory)

## Ohm's Law for Resistors in Parallel:

According to Ohm's law,  $V=I \cdot R$  and in parallel connection of resistances same drop of voltage is there across each resistor. Let  $I_1$  and  $I_2$  currents flows from  $R_1$  and  $R_2$  respectively. So the voltage drop across  $R_1$  is  $V= I_1 \cdot R_1$  and across  $R_2$  is  $V=I_2 \cdot R_2$

$$V_T = I_1 \cdot R_1 \text{ or } I_2 \cdot R_2$$

$$\text{And } I_T = I_1 + I_2$$

$$V_T / R_{eq} = V / R_1 + V / R_2 \quad R_{eq} = (R_1 R_2) / (R_1 + R_2)$$

$$I_T = V_T / R_{eq}, \text{Therefore}$$

$$R_{eq} = (R_1 \cdot R_2) / (R_1 + R_2)$$

# Ohm's Law for Resistances in Parallel (Simulated Data):


## INSTRUCTION

## EXPERIMENTAL TABLE

Resistance( $R_1$ ): 1000  $\Omega$   
Resistance( $R_2$ ): 15  $K\Omega$   
Resistance( $R_{eq}$ ): 0.149977  $\Omega$

Serial No.	Voltage(Volt) V	Current(milliAmpere) mA
1	5	5.33
2	10	10.7
3	12	12.8
4	15	16.0
5	20	21.3
6	25	26.7

## Ohm's Law Parallel

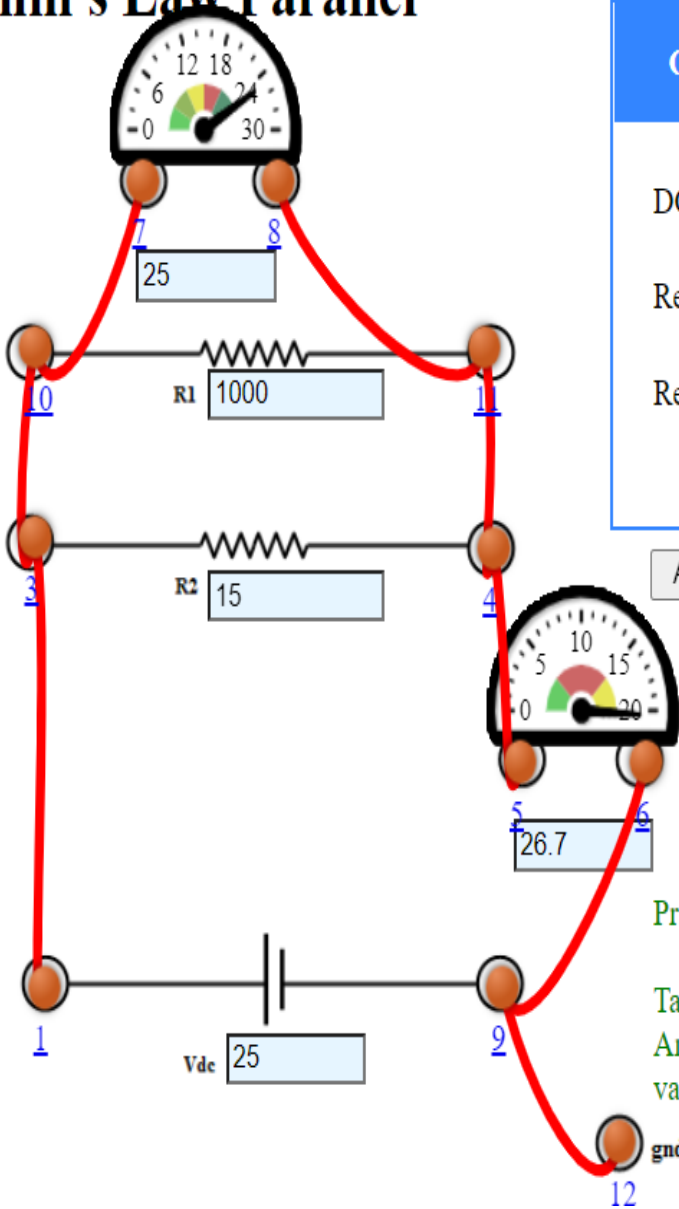

## CONTROLS

DC volt :  Volt  
Resistance1 :  Ohms  
Resistance2 :  Kohms

Add to Table

Plot

Clear

Check  
connection

Delete all  
connection

Print It


Take another sets of Voltmeter and  
Ammeter readings for another Resistance  
value

# Ohm's Law for Resistances in Parallel (Graph)

GRAPH PLOT



V-I Plot

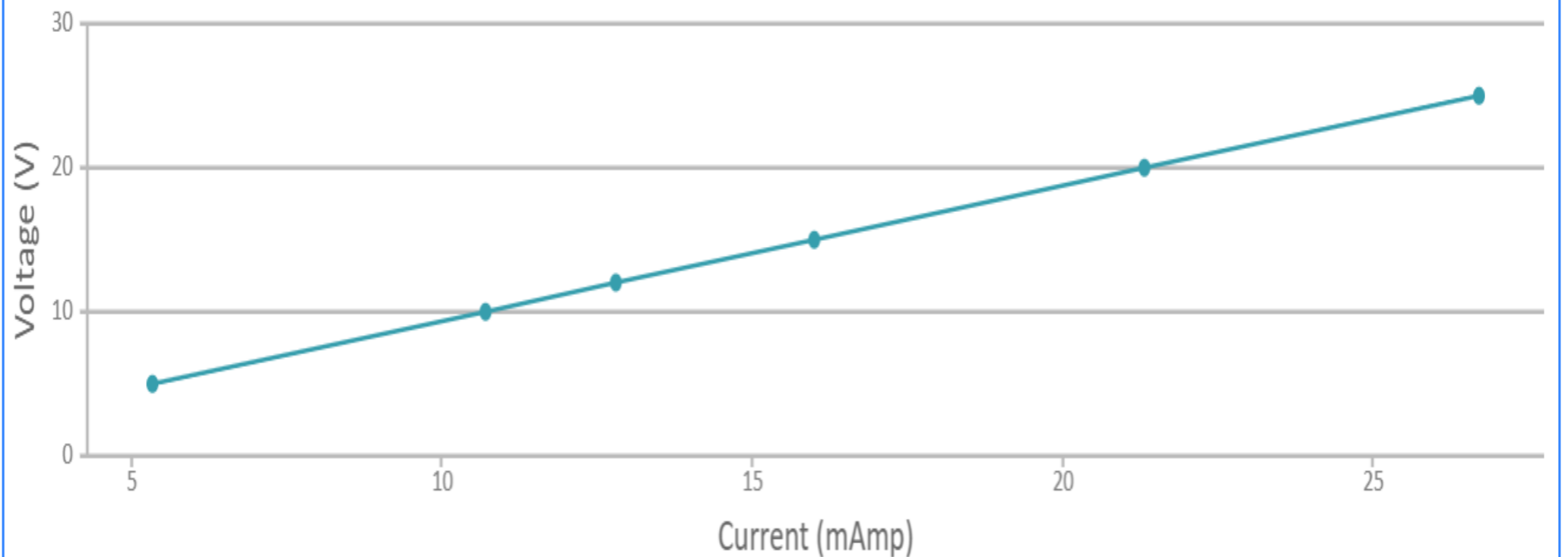

# Non Ohmic Devices( Circuit diagram)

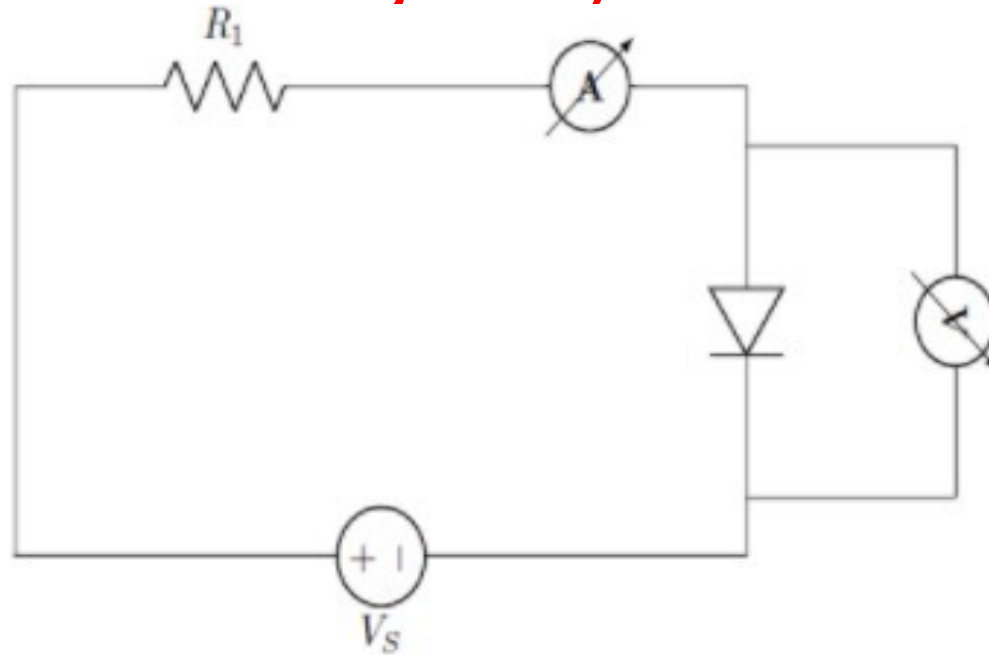


Figure 5: Non Ohmic Device

## Working principle of Non Ohmic Device

A Non ohmic device is a device that does not obey Ohm's Law. Such devices do not have a constant resistance and the resistance is constantly changing also known as dynamic resistance. The value of resistance depends temperature and many other factors. Examples of such devices are tungsten filament (bulb), diode, thermistor etc.


# Non Ohmic Devices (simulated data):

## INSTRUCTION

### EXPERIMENTAL TABLE

Serial No.	Voltage(Volt)	Current (mAmp)	Resistance (KOhm)
1	0.461	0.0500	100
2	0.468	0.0667	75
3	0.478	0.0980	51
4	0.498	0.208	24
5	0.521	0.500	10

## Non Ohmic Device

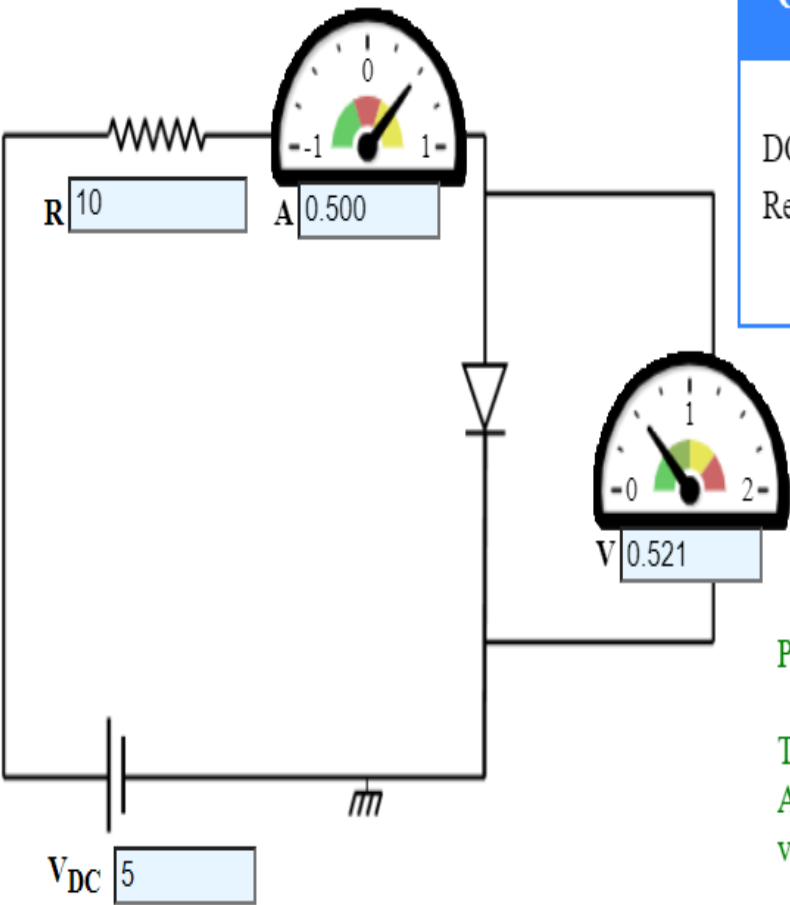

## CONTROLS

DC volt :  Volt  
Resistance :  Kohms

Add to Table

Plot

Clear

Print It

Take another sets of Voltmeter and  
Ammeter readings for another Resistance  
value




# Non Ohmic Resistors (Graph):

GRAPH PLOT



V-I Plot

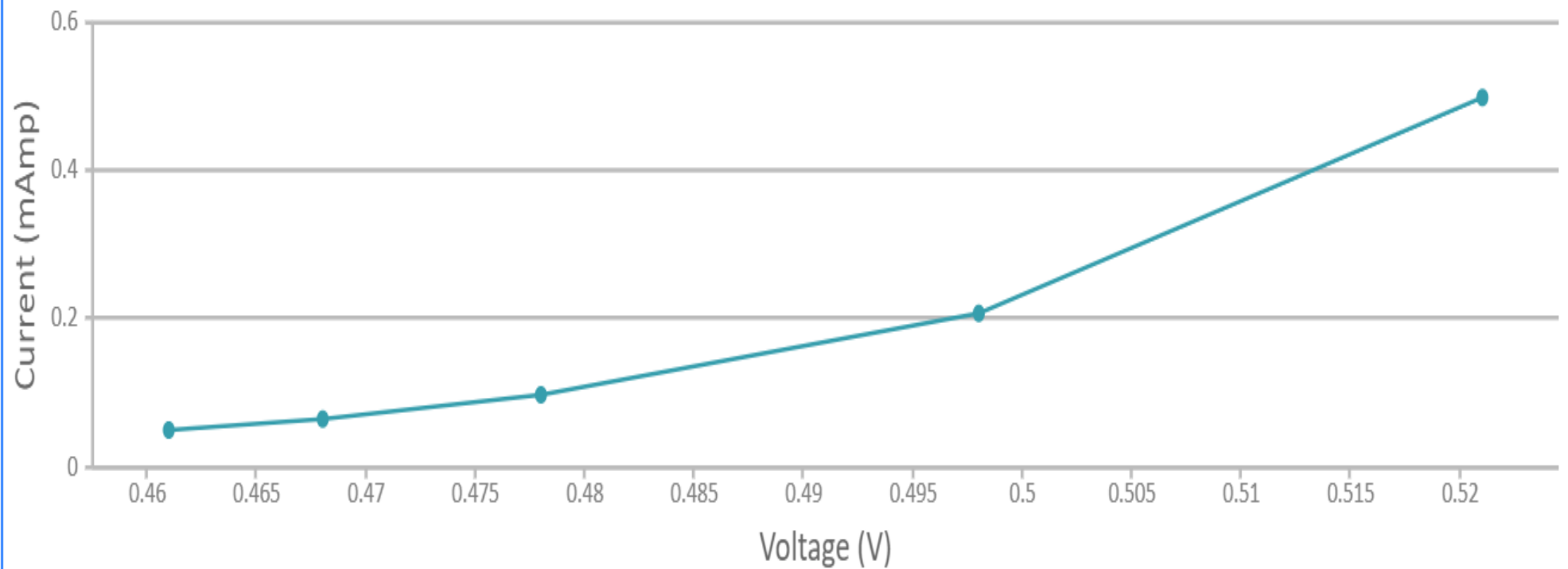


# Summary And Observations:

- In this experiment, we verified Ohm's law for a single Resistor.
- We also found the  $R_{eq}$  for series combination of resistances using Ohm's Law and verified the formula for equivalent resistance for two resistors in series.
- We also found the  $R_{eq}$  for parallel combination of resistances using Ohm's Law and verified the formula for equivalent resistance for two resistors in parallel
- We also verified the working principle of a non ohmic device using simulations and proved that they do not follow ohm's law.
- Also the ammeter and voltmeter used will also have some resistance.

# Part -2

**AIM:** To explain RC Voltage Dividers, working of a RC Circuit as a Low Pass Filter and also working of a RC Circuit as a High Pass Filter
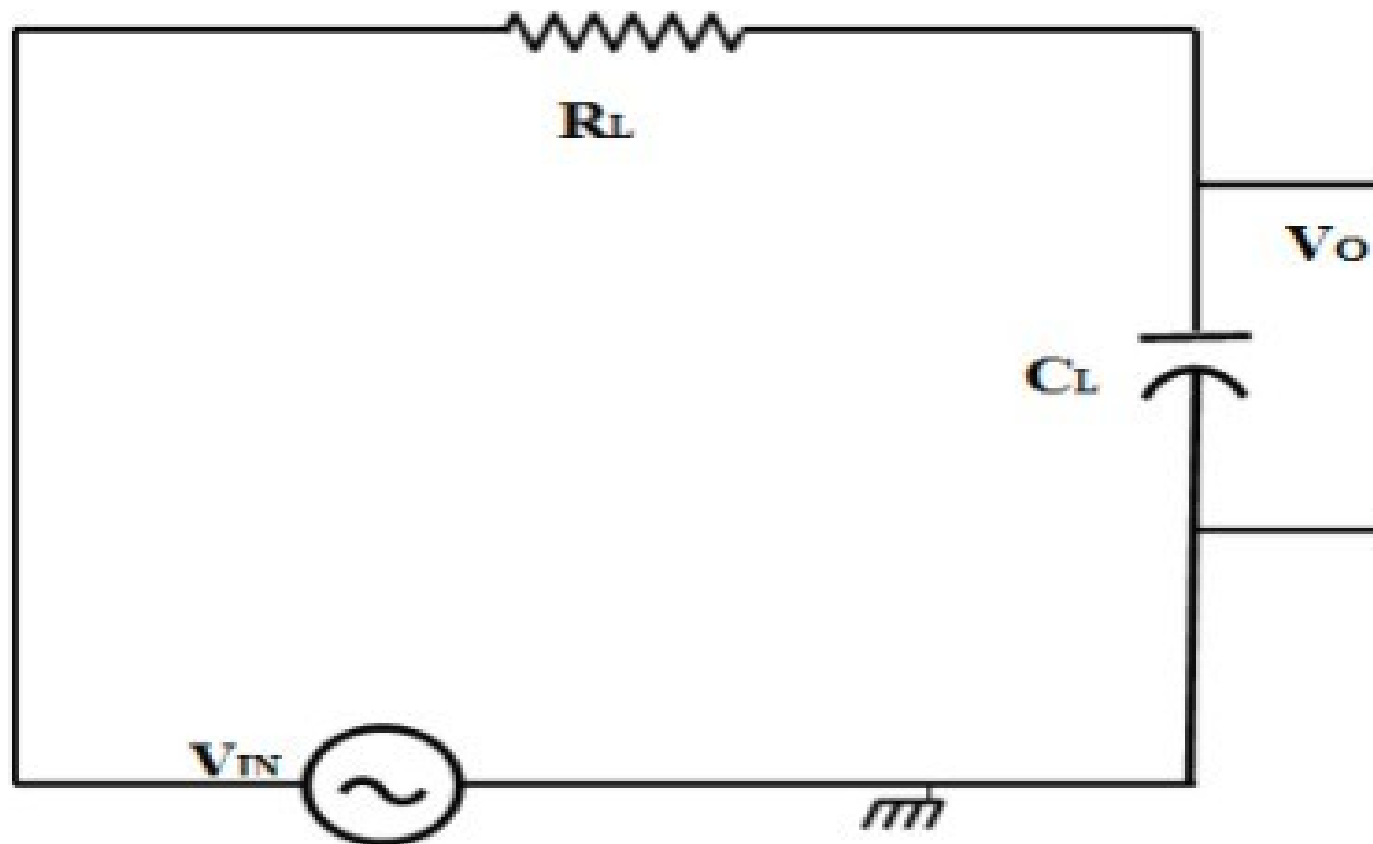
## Circuit Diagram for RC Low Pass Filters



## Working principle of a low pass filter

- **Filters** : A filter is a circuit capable of passing (or amplifying) certain frequencies while removing other frequencies. Thus, a filter can extract the required frequencies from signals and remove the undesirable or irrelevant frequencies.
- **Low Pass Filters** : This type of filters allows only the frequency lower than the cut off frequency( $f_c$ ), starting from zero. This is made by connecting a resistor in series with a capacitor and output voltage is measured across the capacitor.
- **Cut-Off Frequency**: The frequency at which the amplitude of the signal is decreased by 3 decibels is known as the cut off frequency( $f_c$ ). At this value power reduces by 50 percent.(or output voltage is half the input voltage).  
 , so this is the reason for selecting 3 decibels as reference. Formula  
 $(f_c = \frac{1}{2\pi R_L C_L})$

- $X_C = \frac{1}{2\pi f C}$  a:(C:Capacitance,f:Frequency)

- Low-Pass Filter Phase Shift: Phase =  $-\arctan(2\pi \times f \times R \times C)$
- $V_{out}$  : Voltage difference across the capacitor.


$$V_{OUT} = V_{IN} \left( \frac{X_C}{\sqrt{R_1^2 + X_C^2}} \right)$$

Here as we decrease the frequency , the capacitive reactance increases as it is inversely proportional to the frequency and thus transferring the whole input voltage as output, and at higher frequencies the voltage is very less and it disallows the higher frequency, therefore at low frequency  $V_{in}=V_{out}$  and making the circuit as a **Low pass filter.**

# Simulated Data for RC Low Pass Filter:

$V_{in}=10\text{ V}$   
 $R_L=10\text{k}\Omega$   
 $C=0.01\text{nF}$

## INSTRUCTION

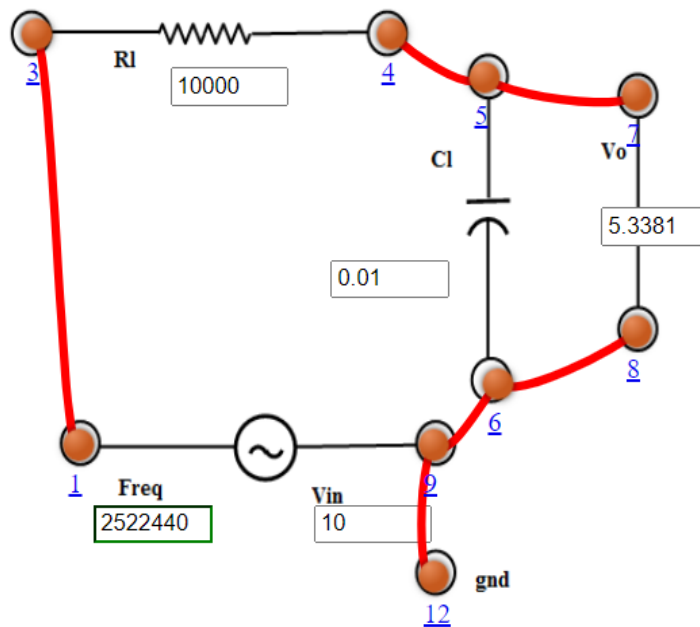

Phase of 1st order low pass filter

## CONTROLS

Load Resistance ( $R_L$ ) :   $\Omega$   
Load Capacitor(  $C_L$ ) :  nF  
Input Voltage ( $V_{in}$ ) :  V  
Frequency (Freq) :  Hz

Add to Table

Phase Response

Clear

Check  
connection

Delete all  
connection

## EXPERIMENTAL TABLE


Serial No.	Frequency(Hz)	Magnitude(dB)	Phase(theta)	Output Voltage(V)
1	50	-4.33854e-9	-0.00181185	10.000
2	149	-3.7787200000000004e-8	-0.00534715	10.000
3	438	-3.29112e-7	-0.0157806	10.000
4	3818	-0.0000249656	-0.137443	10.000
5	11267	-0.000217436	-0.405616	9.9997
6	33252	-0.001893432	-1.19691	9.9978
7	98134	-0.01646342	-3.52837	9.9811
8	289614	-0.1413372	-10.3134	9.8386
9	854713	-1.099534	-28.2394	8.8110
10	2522440	-5.45226	-57.7660	5.3381

# Graph for RC Low Pass Filter(Frequency Response)

GRAPH PLOT



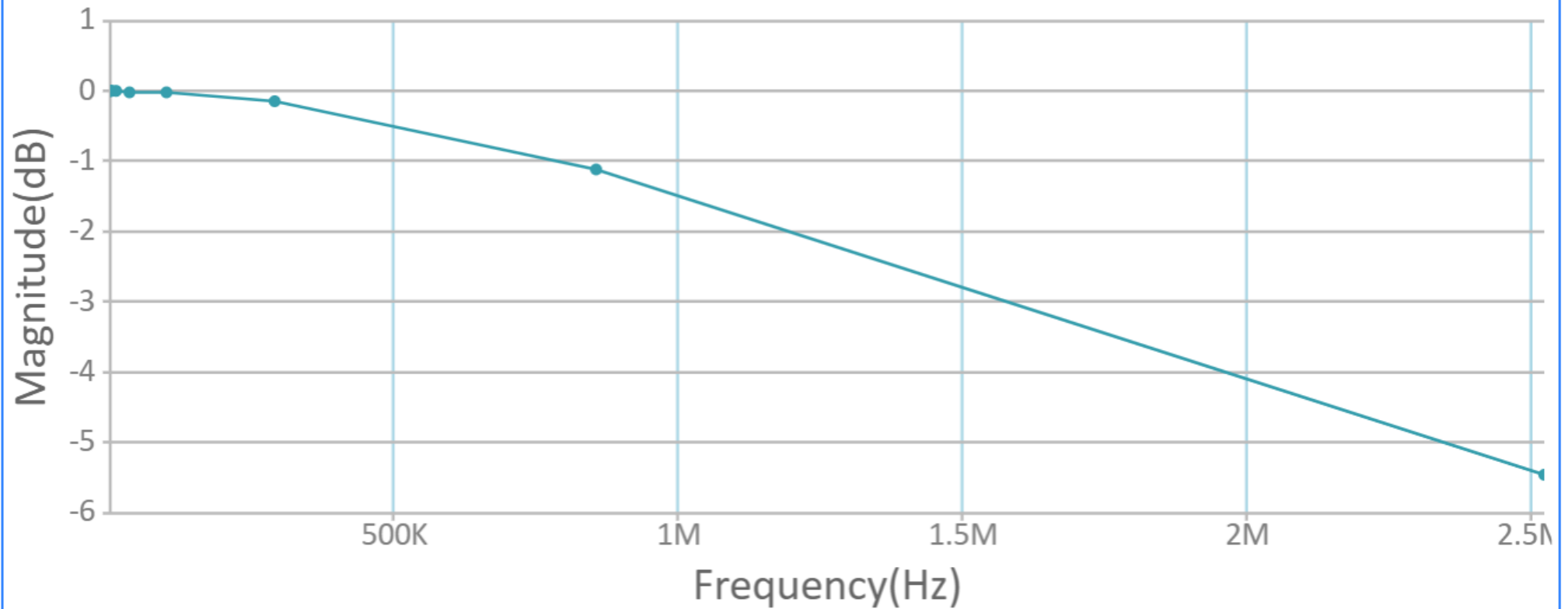
## Frequency Response of a 1st Order Low Pass Filter





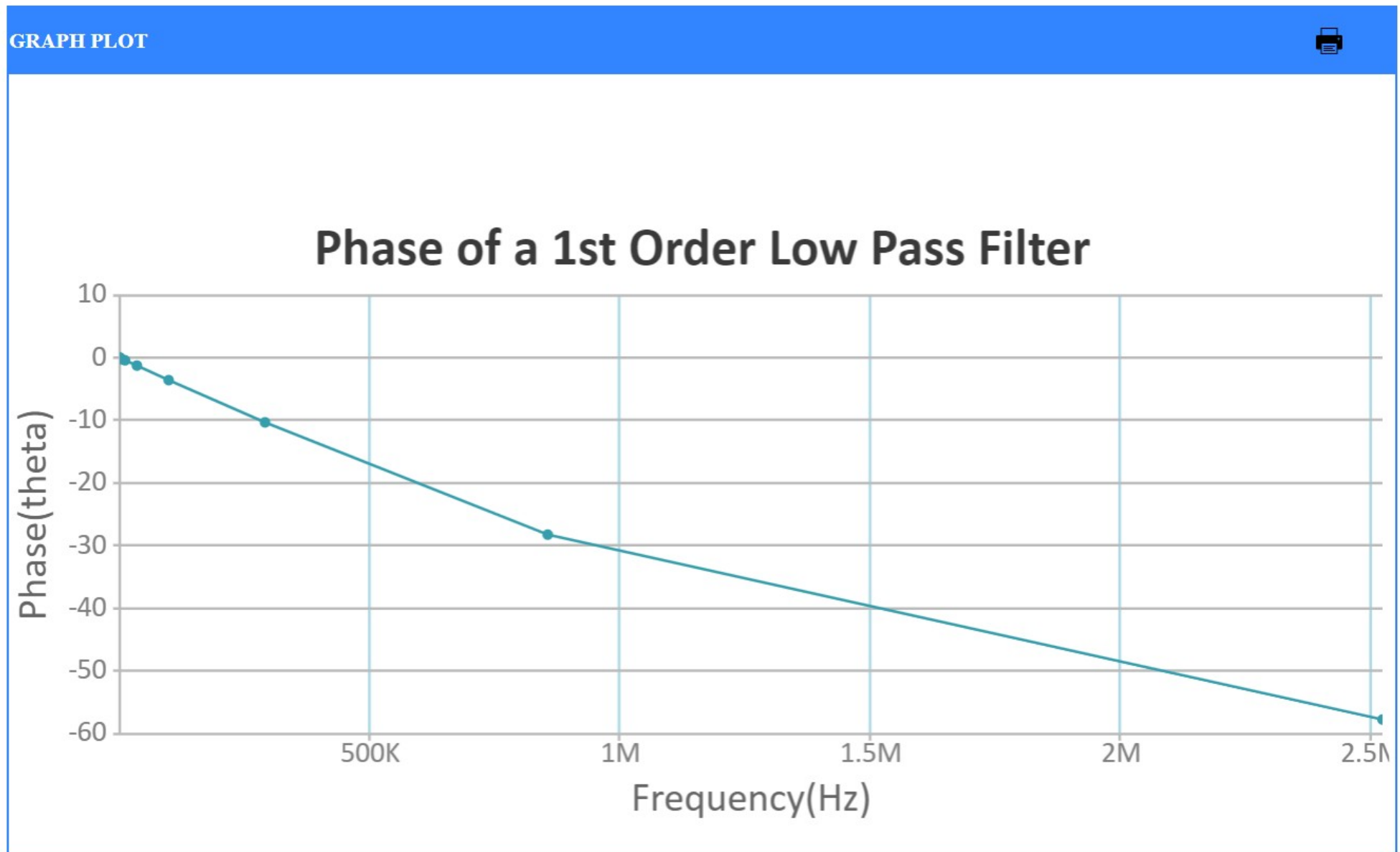
# Graph for RC low pass filter(Phase response)


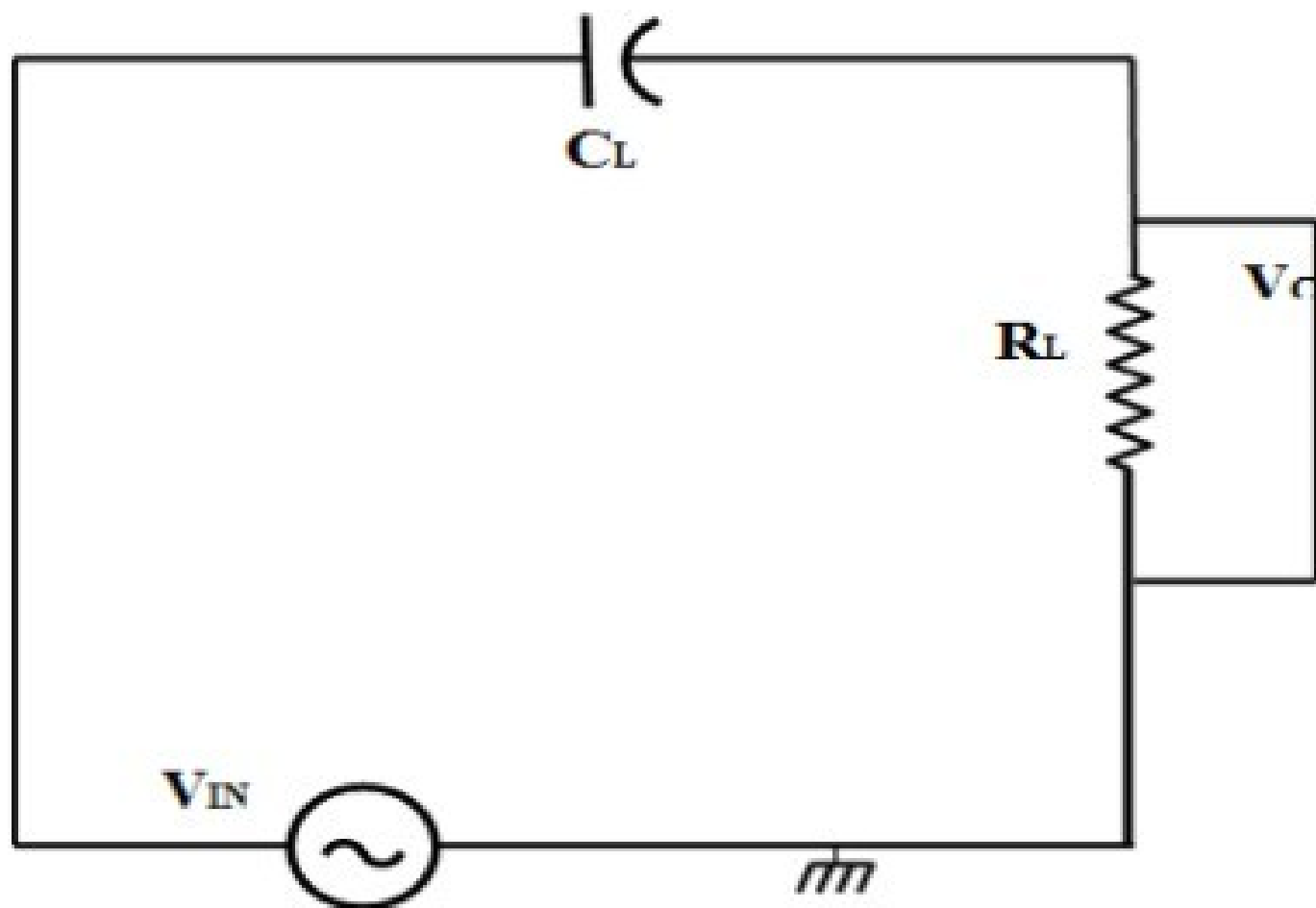
## Circuit Diagram for RC High Pass Filter



## Working principle of high pass filter

- Filters : A filter is a circuit capable of passing (or amplifying) certain frequencies while removing other frequencies. Thus, a filter can extract the required frequencies from signals and remove the undesirable or irrelevant frequencies.
- High Pass Filters : This type of filters allows only the frequency higher than the cut off frequency( $f_c$ ). This is made by connecting a resistor in series with a capacitor and output voltage is obtained across the resistor.
- Cut-Off Frequency: The frequency at which the amplitude of the signal is decreased by 3 decibels is known as the cut off frequency( $f_c$ ). At this value power is  $\frac{1}{2}$  of input power, so this is the reason for selecting 3 decibels as reference. Formula  

$$f_c = \frac{1}{2\pi R_L C_L}$$
- Capacitive Reactance:(C:Capacitance,f:Frequency)

$$X_C = \frac{1}{2\pi f C}$$

- High Pass Filter Phase Shift: Phase =  $\pi/2 - \arctan(2\pi f R C)$
- $V_{out}$  : Voltage difference across the resistor.


$$A_V = \frac{V_{OUT}}{V_{IN}} = \frac{R}{\sqrt{R^2 + X_C^2}}$$

Here as we increase the frequency, the capacitive reactance decreases as it is inversely proportional to the frequency and thus almost all the input voltage drops in the resistance, therefore at higher frequency  $V_{in}=V_{out}$  making the circuit as a **high pass filter**.

# Simulated Data for RC high Pass Filter:

$V_{in}=10\text{ V}$   
 $R_L=10\text{kOhm}$   
 $C=1.71\text{nF}$

## INSTRUCTION

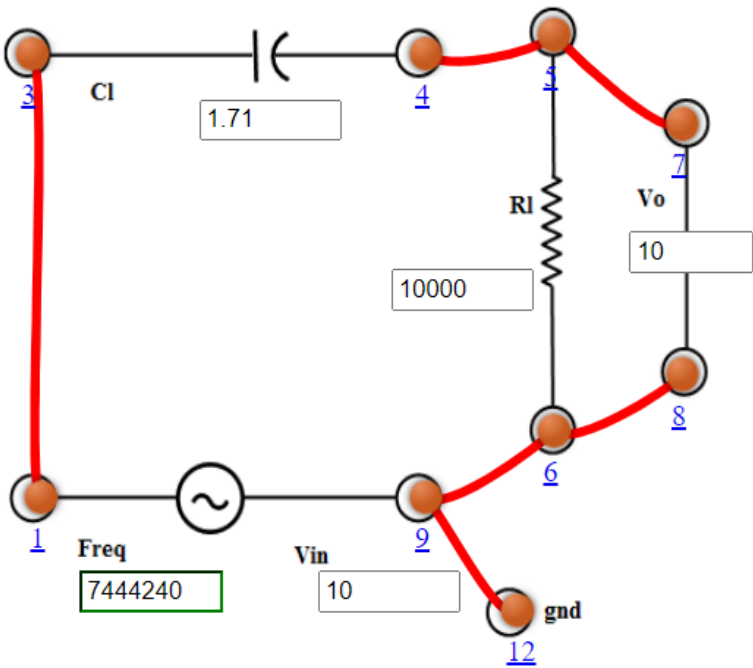

Phase of 1st order low pass filter

## CONTROLS

Load Resistance ( $R_L$ ) :   $\Omega$   
Load Capacitor(  $C_L$ ) :  nF  
Input Voltage ( $V_{in}$ ) :  V  
Frequency (Freq) :  Hz

Add to Table

Phase Response

Clear

Check  
connection

Delete all  
connection

## EXPERIMENTAL TABLE


Serial No.	Frequency(Hz)	Magnitude(dB)	Phase(theta)	Output Voltage(V)
1	50	-45.3446	89.7358	0.054047
2	438	-26.554000000000002	87.3492	0.47021
3	1294	-17.2275	82.1325	1.3760
4	3818	-8.41926	67.7411	3.7935
5	11267	-2.26096	39.5926	7.7082
6	98134	-0.03893	5.42336	9.9553
7	289614	-0.00448756	1.84254	9.9948
8	854713	-0.000515474	0.624525	9.9994
9	2522440	-0.0000591872	0.211624	9.9999
10	7444240	-0.000006795660000000001	0.0717078	10.000
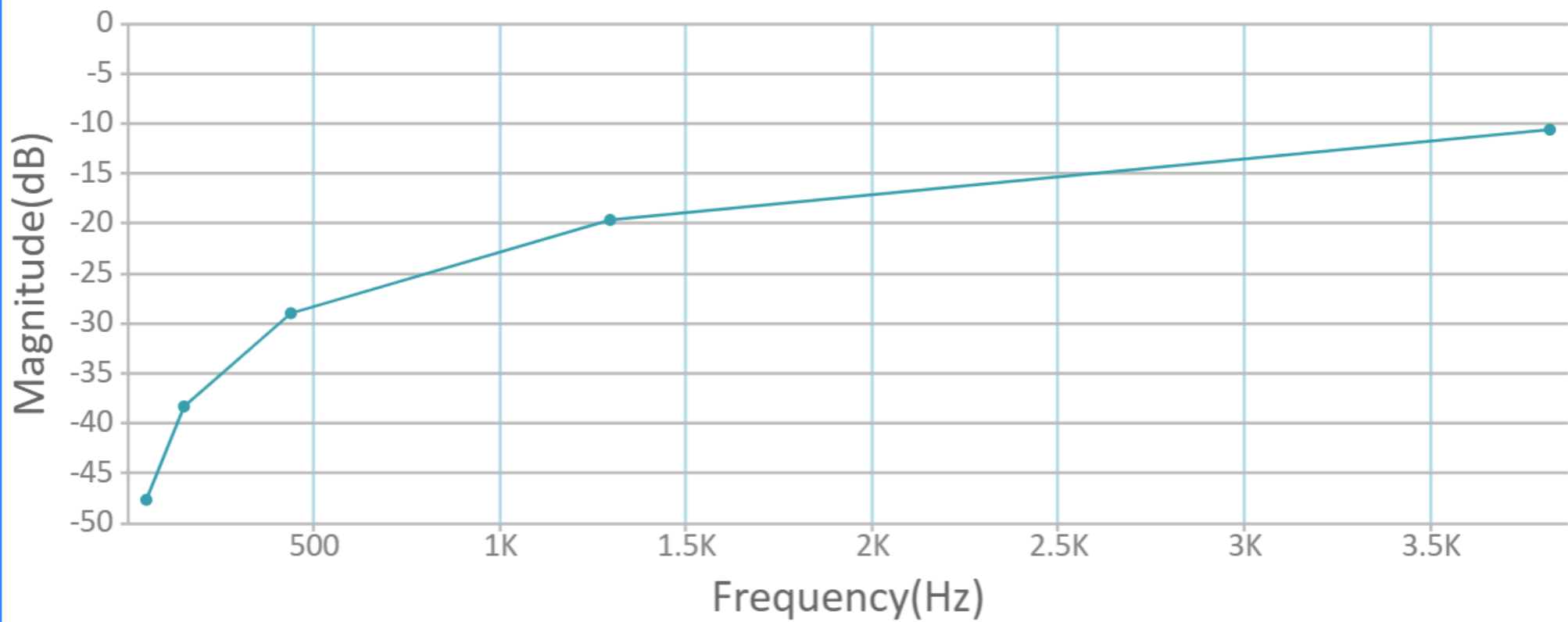
# Frequency response graph for RC high Pass Filter

GRAPH PLOT



Frequency Response of a 1st Order High Pass Filter




# Phase response graph for RC high Pass Filter

GRAPH PLOT



CanvasJS Trial

## Phase of a 1st Order High Pass Filter

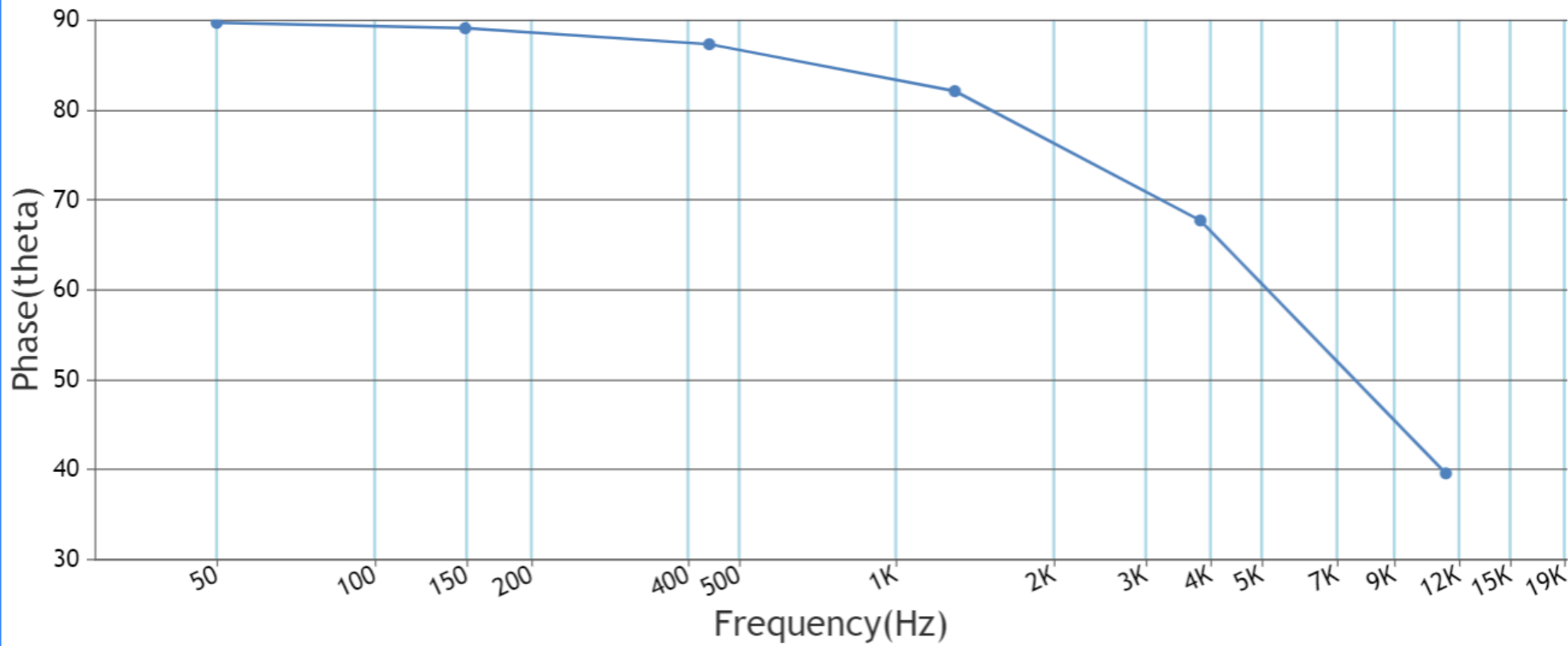

# Summary

- In this experiment, we learnt what is an electrical filter and how it works.
- Secondly, we saw the construction and working of the Low Pass Filter and how it disallows the higher frequencies
- Next, we saw the construction and working of the High Pass Filter and how it allows higher frequencies only.

## Observations


1. The plot for frequency response and phase response is better depicted in the vlab simulation where the circuit is pre drawn.
2. In practical the output frequency response is not a square wave but a curve.



# Part -3

**AIM:** To study the working of an RC circuit as a differentiator and integrator and thereby study the output response to a square wave input.
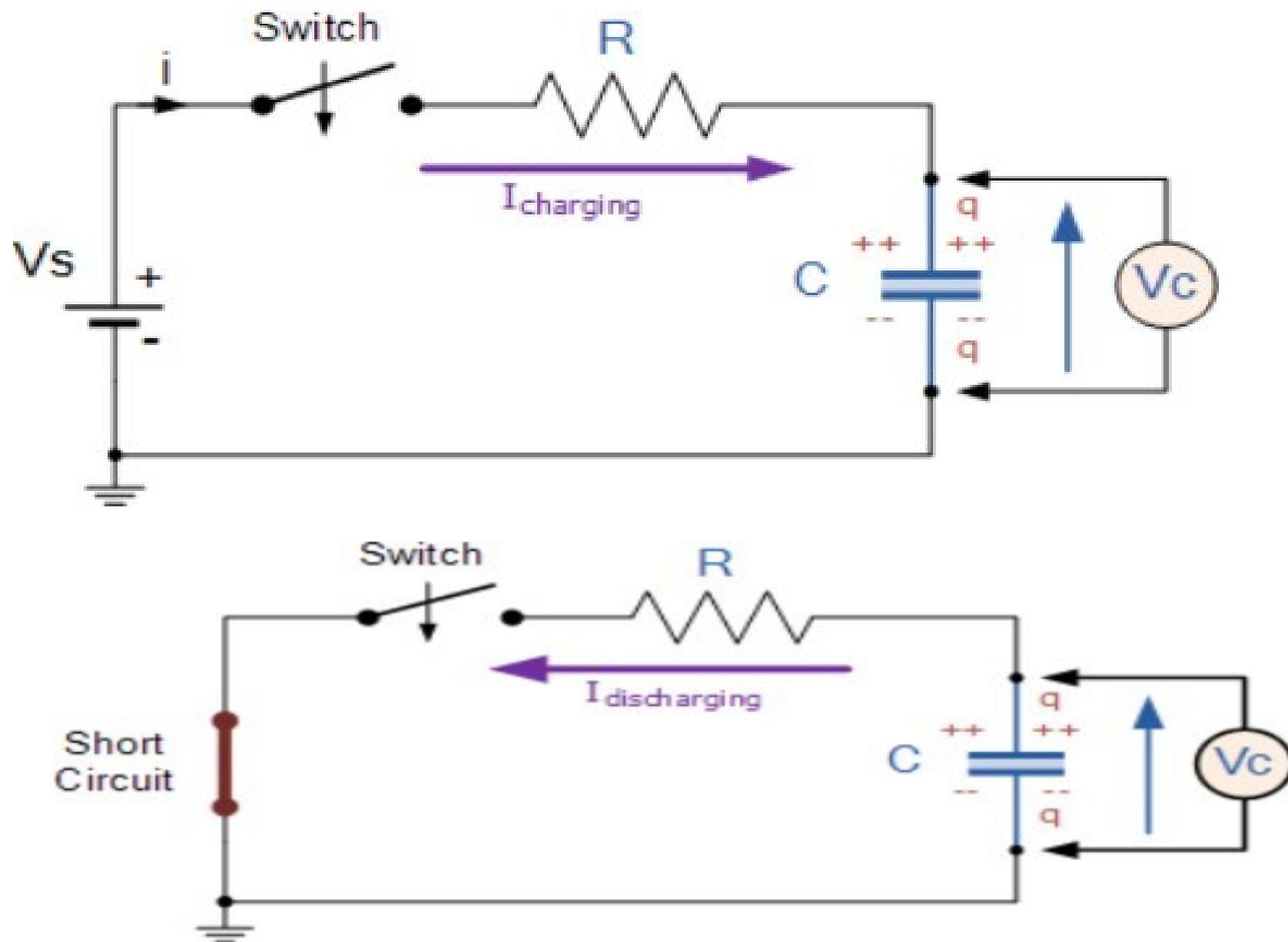
# Circuit Diagram for RC Circuits charging and discharging



# Charging and Discharging of capacitor(Theory)

- Charging Of Capacitor

- In the first circuit ,a battery is supplying energy to the capacitor in the form of charge carried in the form of current from the battery.

- Kirchoff's Equation for charging the capaci  $V_s - R \times i(t) - V_c(t) = 0$

- Using this formula ,we can find the potential difference across the capacitor as (keeping  $i(t)=dq/dt$  and  $V_c(t)$  as  $q/C$ ,where  $q$  is charge on capacitor and  $C$  is capacitance of the capacitor) :

$$V_C = V_S (1 - e^{(-t/RC)})$$

- Here as we can see from the equation, Voltage increases ,and thus charge increases, with time ( $t$ ) making it a charging circuit.

- Here  $R \times C$  is the time constant for the circuit.

- In 1 time constant  $\times R \times C$  , the capacitor charges 63% of the maximum charge that can come in this circuit.

- Discharging of Capacitor


- In the second circuit ,capacitor is supplying energy to the resistor in the form of current and heat energy is produced, thus discharging the capacitor.

- Kirchoff's Equation for discharging the capacitor:  $\times$

$$V_c(t) = i(t) \times R$$

- Using this formula ,we can find the potential difference across the capacitor as (keeping  $i(t)=dq/dt$  and  $V_c(t)$  as  $q/C$ ,where  $q$  is charge on capacitor and  $C$  is capacitance of the capacitor) :
- Here as we can see from the equation, Voltage decreases ,and thus charge decreases  $V_C = V_S \times e^{-t/RC}$  (t) making it a discharging circuit.
- Here also  $R \times C$  is the time constant for the circuit.
- In 1 time constant  $= R C$  , the capacitor charges 63% of the charge it had at starting.
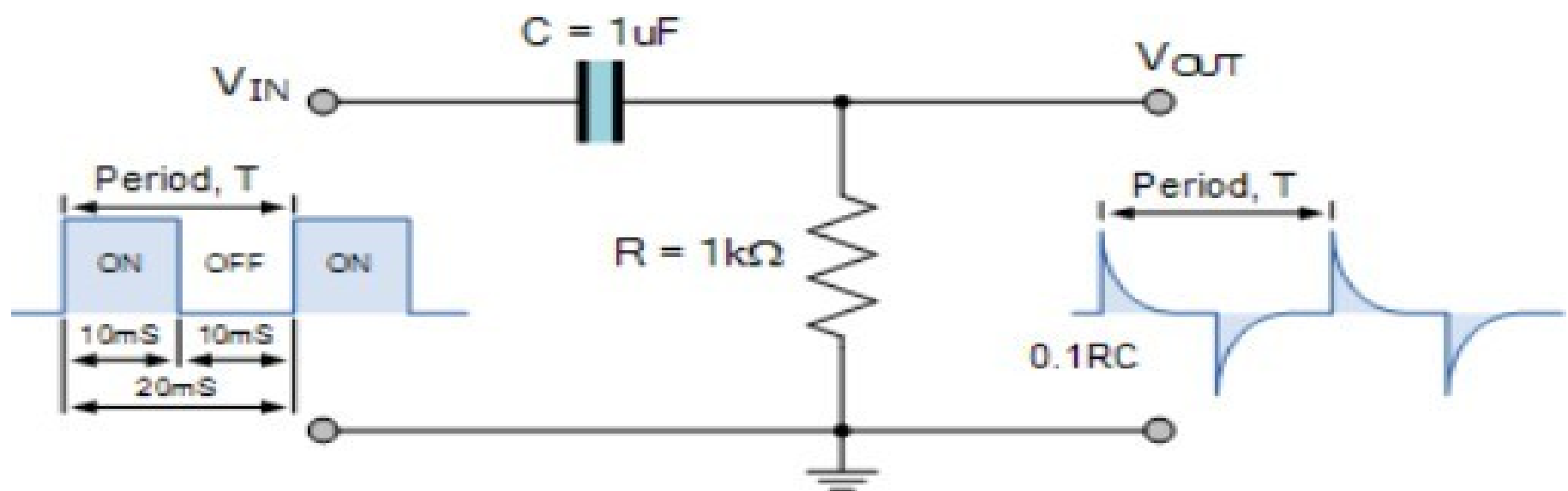
## Circuit Diagram for RC Circuits as differentiator




## Working principle of RC differentiator circuits

- The Differentiator circuit converts or 'differentiates' a square wave input signal into high frequency spikes at its output.
- As shown in the circuit ,a capacitor and a resistor is joined in series and a voltmeter is attached to the ends of the resistor.
- In an RC circuit if we take the voltage drop across R, and if we keep RC time constant as very short compared to the time period of the input waveform we will be differentiating the square wave.
- $RC \ll \text{Time period of input waveform.}$

# Oscilloscope simulations for RC differentiator circuit

## INSTRUCTION

### OSCILLOSCOPE

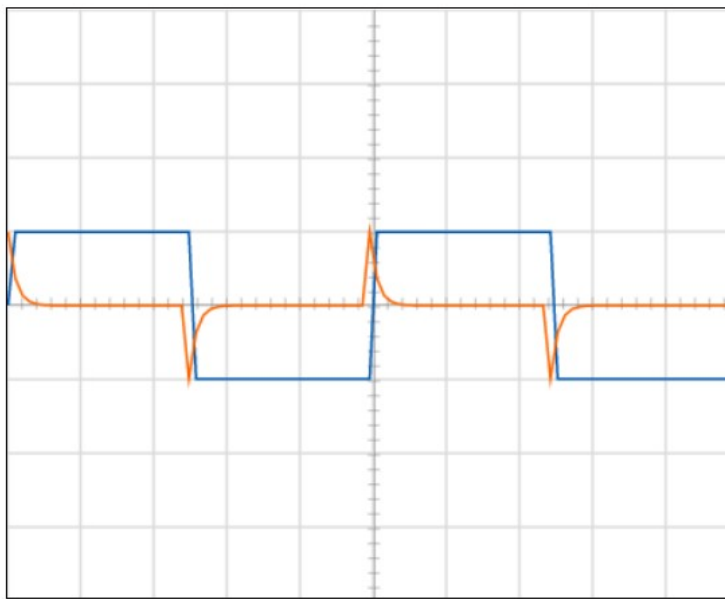

Channel 1


Channel 2

Ground


Dual



## CIRCUIT

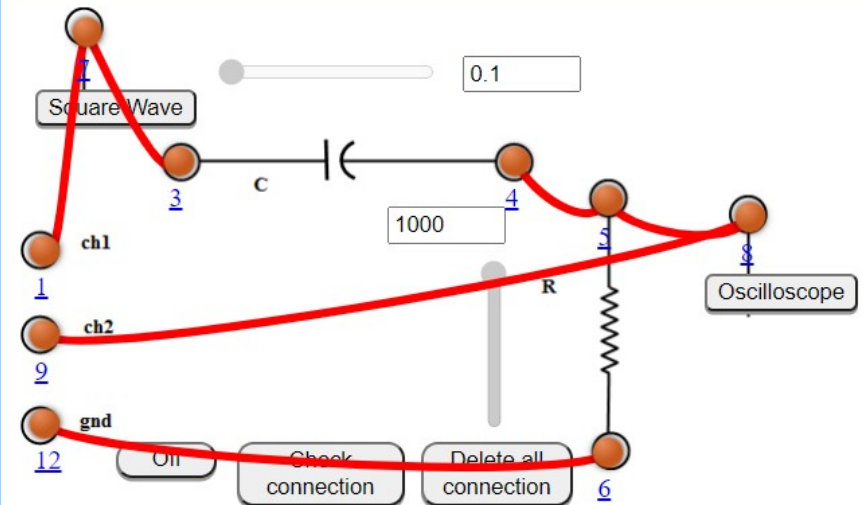


## CONTROLS

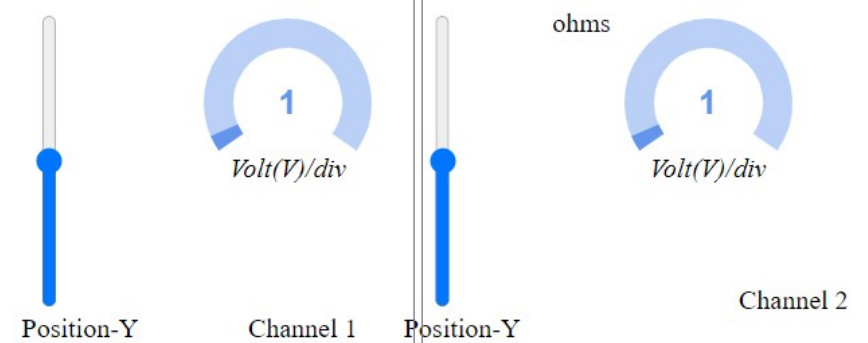

# Oscilloscope simulations for RC differentiator circuit

## INSTRUCTION

## OSCILLOSCOPE

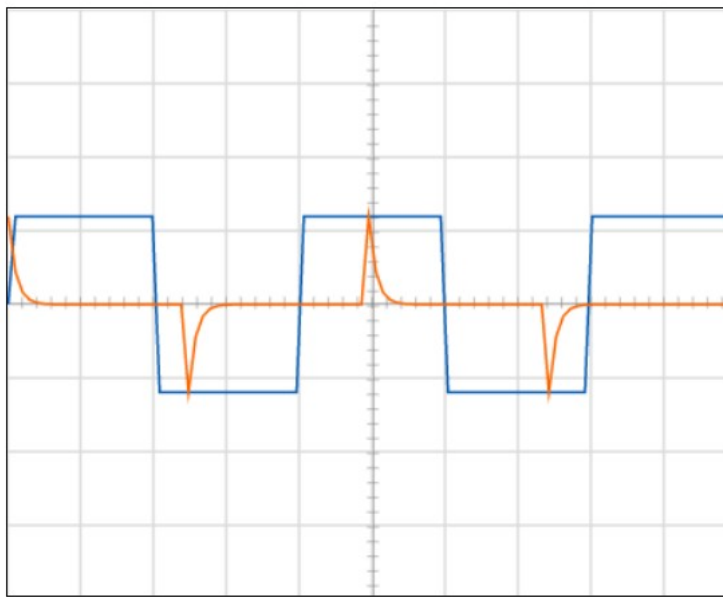

Channel 1

Channel 2


Ground

Dual


2500  
Frequency(Hz)

1.3  
Amplitude(Volt)

## CIRCUIT

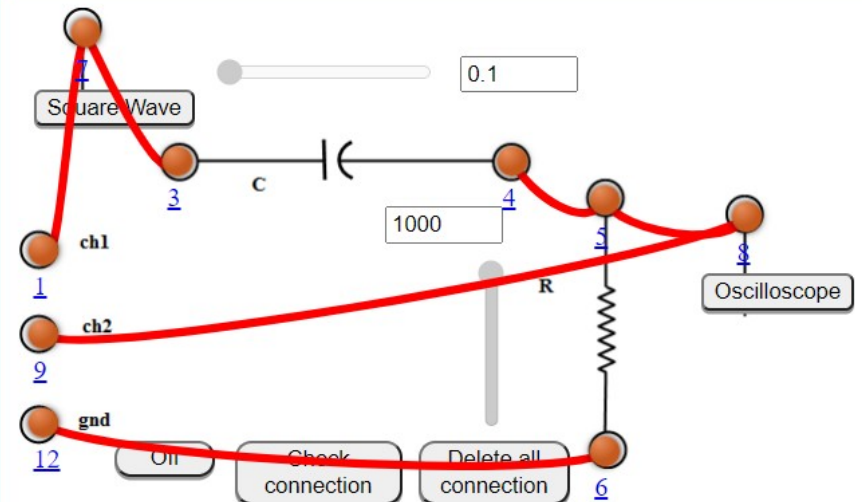

## CONTROLS

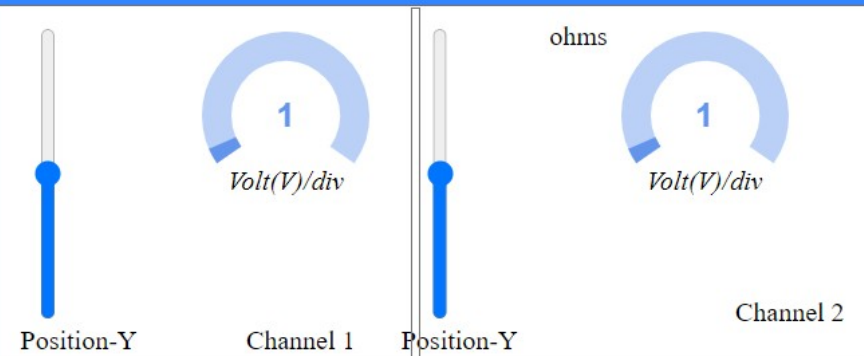




# Oscilloscope simulations for RC differentiator circuit

INSTRUCTION

OSCILLOSCOPE

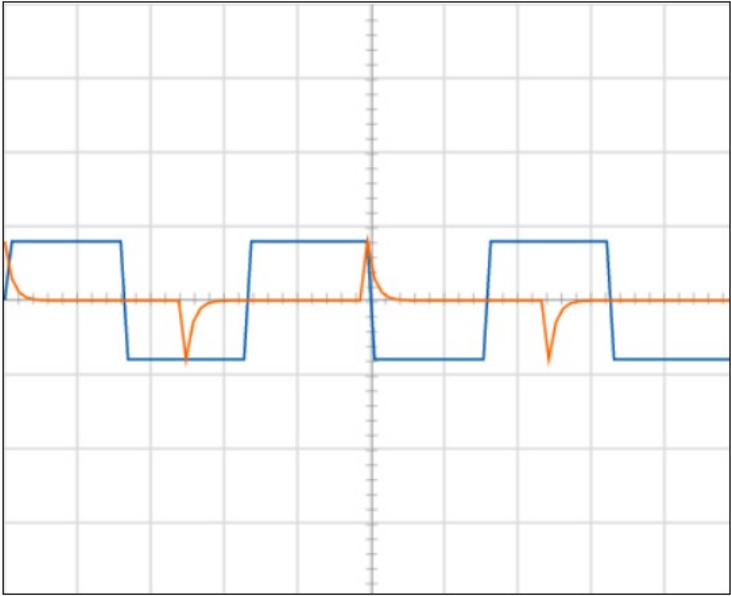

Channel 1

Channel 2

Ground

Dual


3000

Frequency(Hz)

0.9

Amplitude(Volt)

CIRCUIT

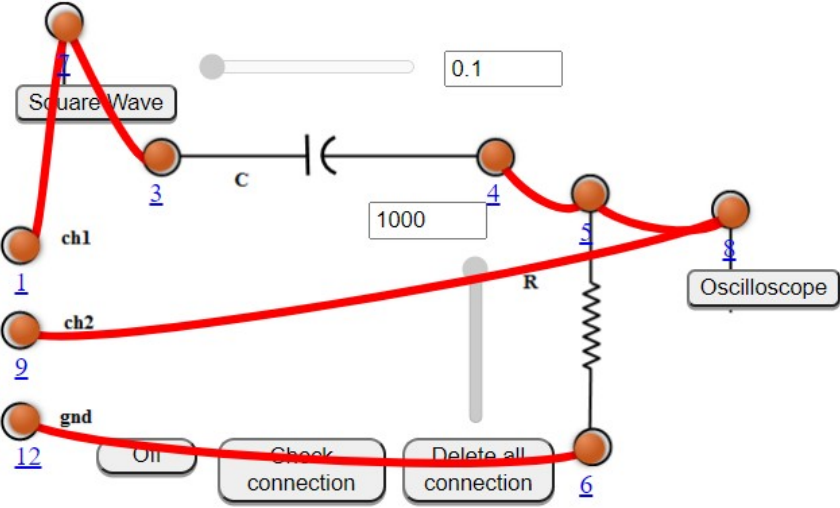

Controls

Position-Y

Channel 1

1

Volt(V)/div

Position-Y

Channel 2


1

Volt(V)/div

# Oscilloscope simulations for RC differentiator circuit

## INSTRUCTION

## OSCILLOSCOPE

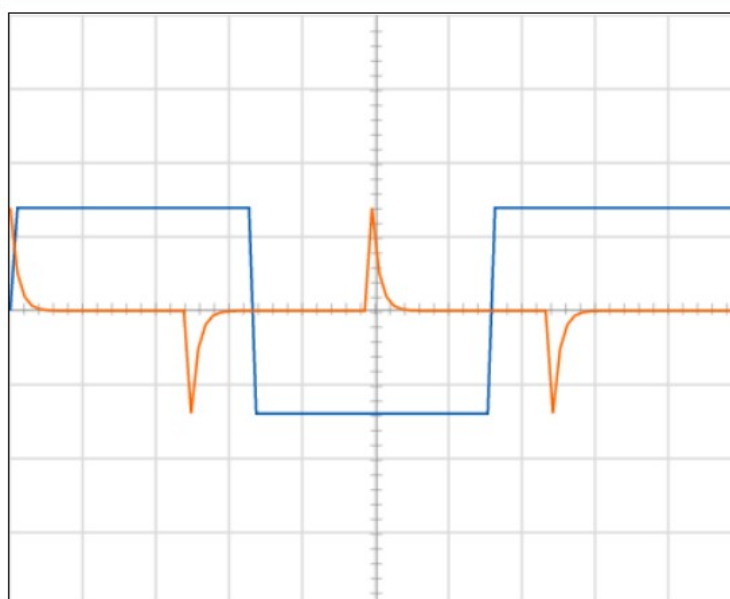


Channel 1


Channel 2

Ground


Dual

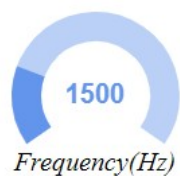


## CIRCUIT

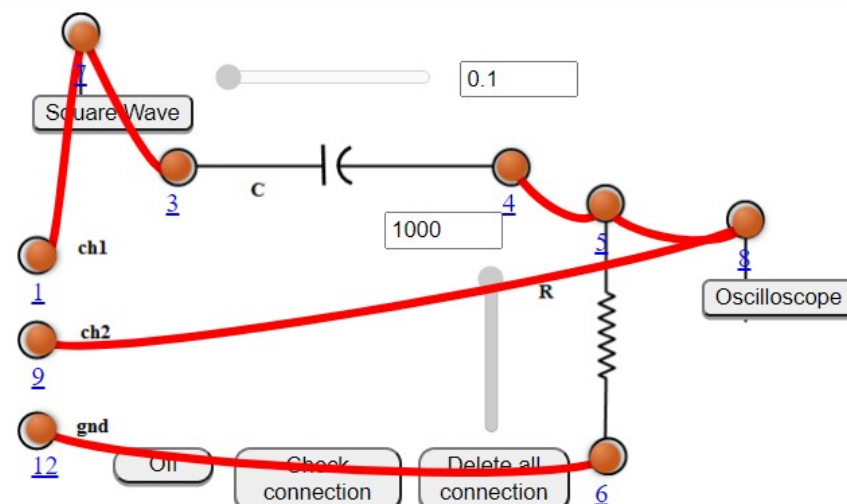

## CONTROLS

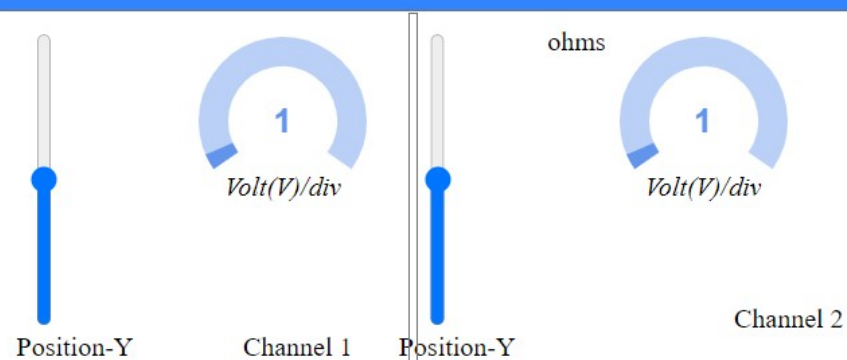
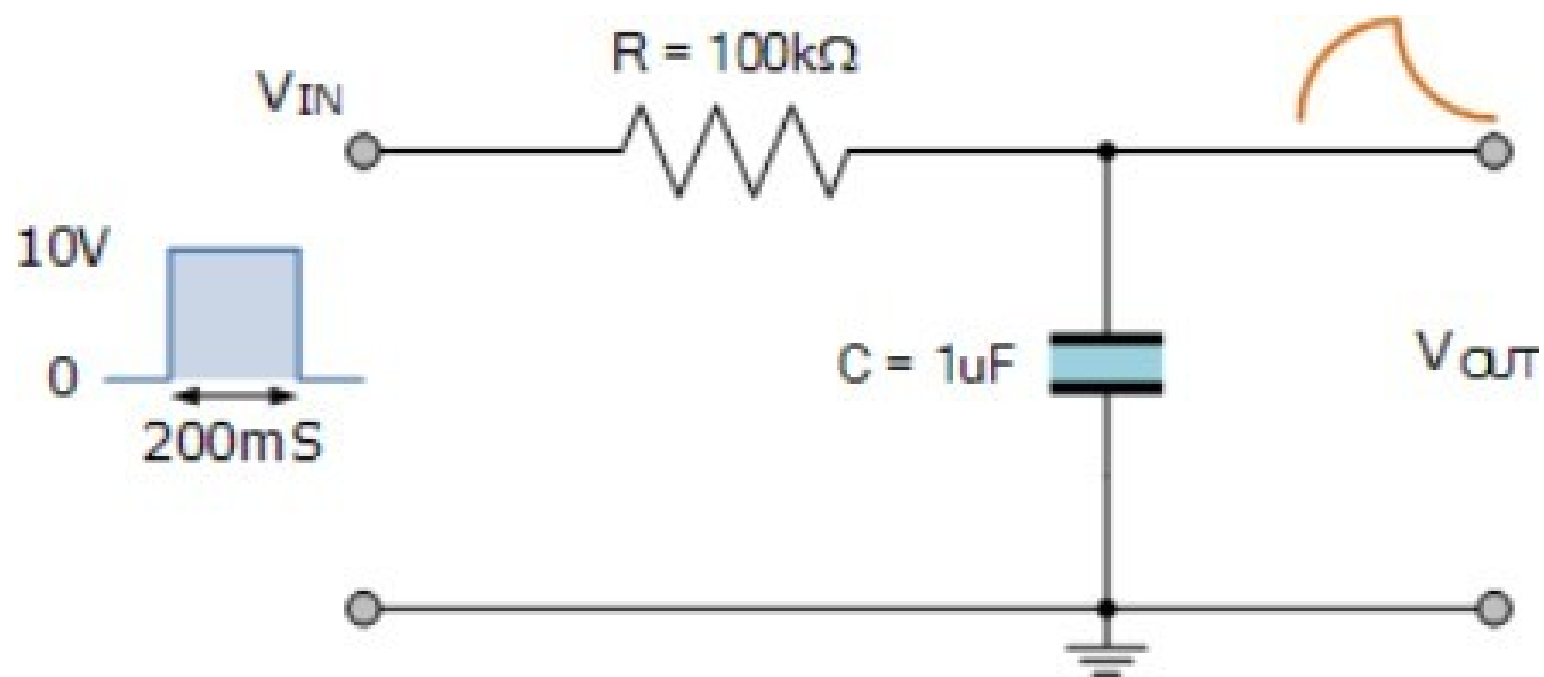
## Circuit Diagram for RC Circuits as integrator



# Working principle of RC integrator circuits


- The Integrator circuit converts or 'integrates' a square wave input signal into triangular waveforms at its output.
- As shown in the circuit above, a capacitor and a resistor is joined in series and a voltmeter is attached to the ends of the capacitor.
- So, we put a resistor such that we can control the current and ideally try to have  $dV_{out}/dt$  to be a constant. Since the current does not change much during the initial part of the charging and discharging of the capacitor, the value of  $RC$  must be chosen such that it is large compared to the time period of the square wave.
- $RC \gg$  Time period of square wave.

# Oscilloscope simulations for RC integrator circuit

## RC Integrator

### INSTRUCTION

### OSCILLOSCOPE


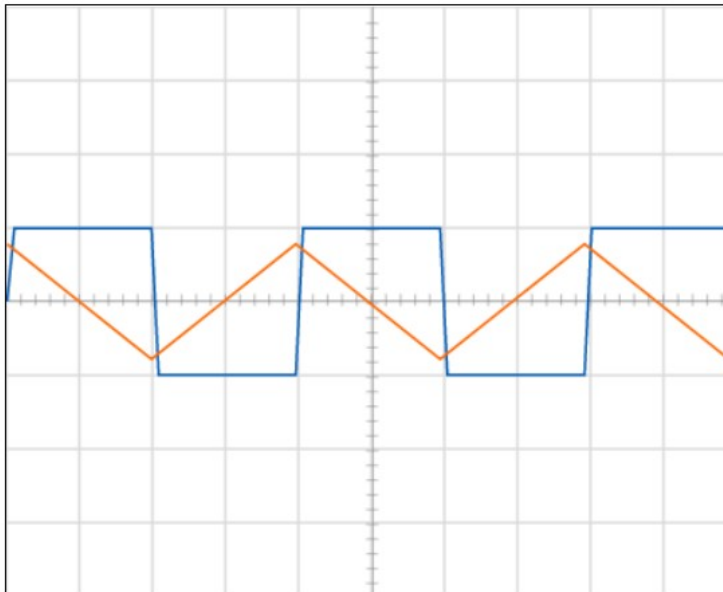


Channel 1


Channel 2

Ground


Dual

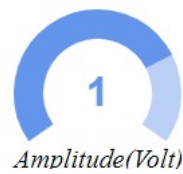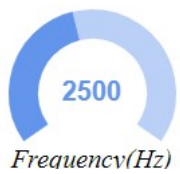

### CIRCUIT

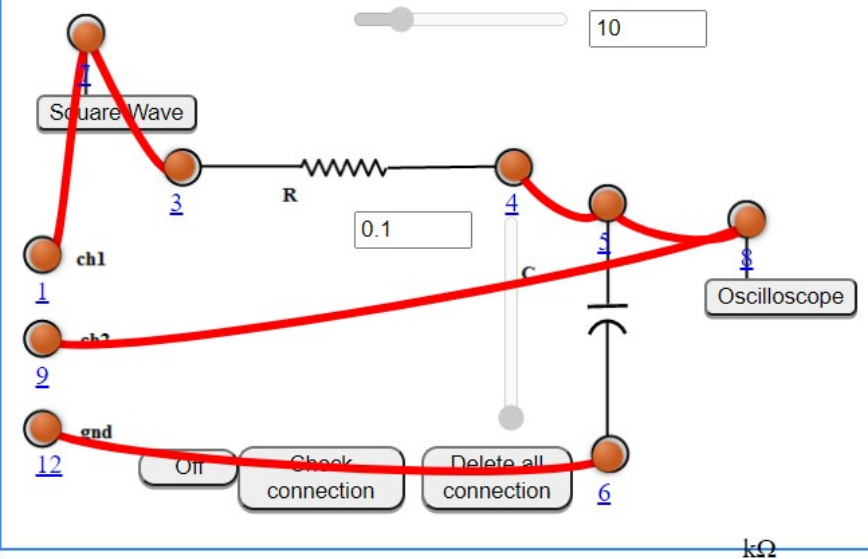


### CONTROLS

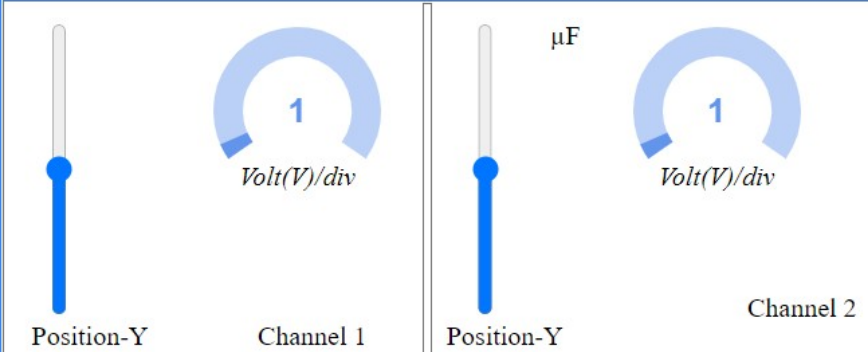

# Oscilloscope simulations for RC integrator circuit

## OSCILLOSCOPE

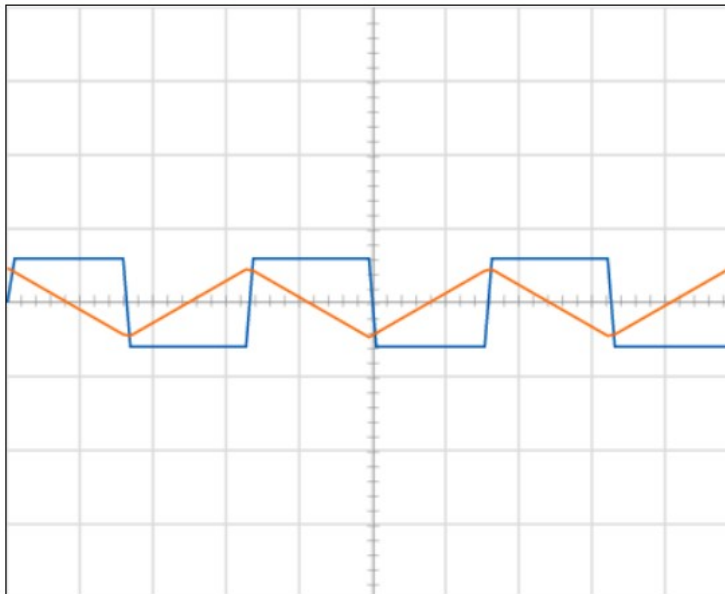

Channel 1


Channel 2

Ground


Dual

3000  
Frequency(Hz)

0.6  
Amplitude(Volt)

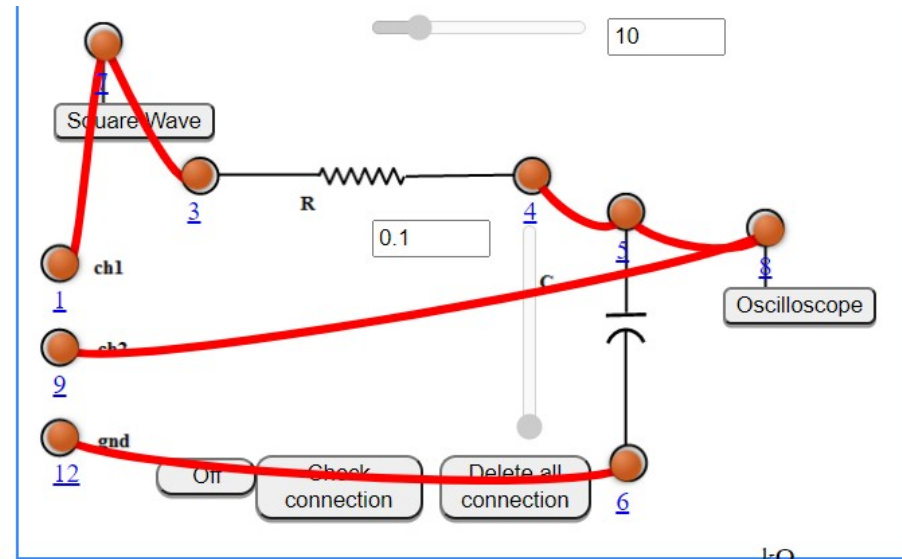


## CONTROLS

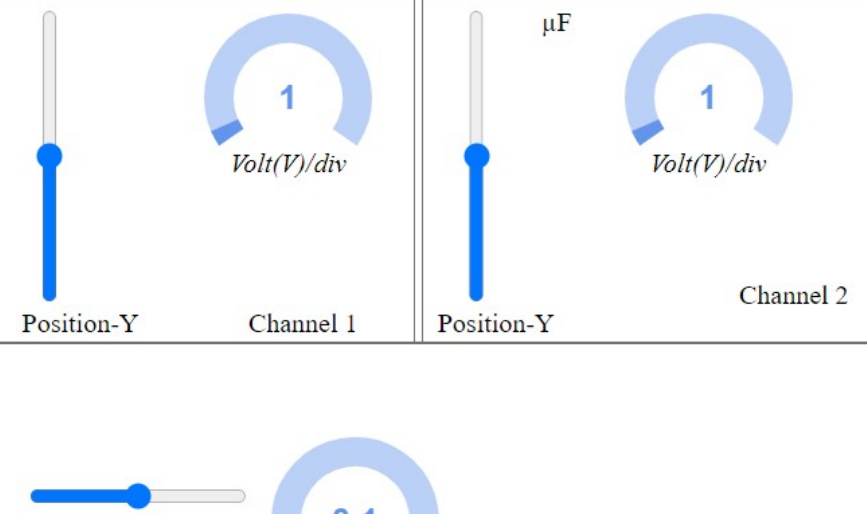

# Oscilloscope simulations for RC integrator circuit

## OSCILLOSCOPE

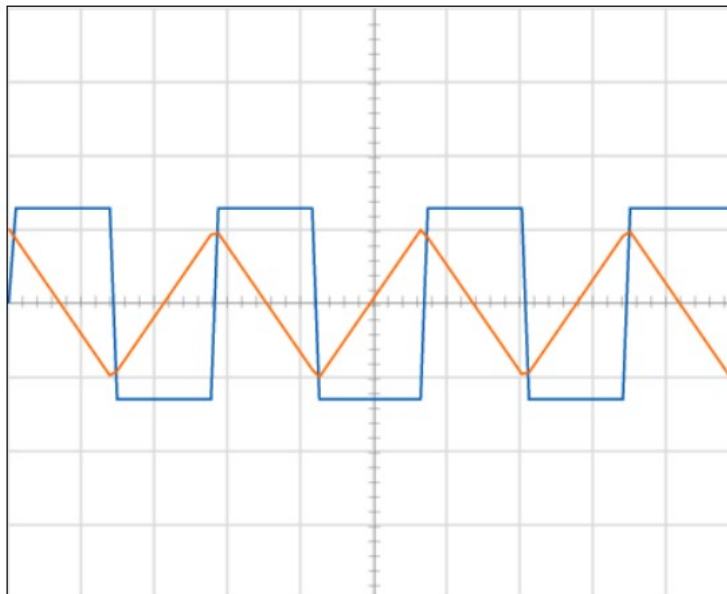

Channel 1


Channel 2

Ground


Dual

3500  
Frequency(Hz)

1.3  
Amplitude(Volt)

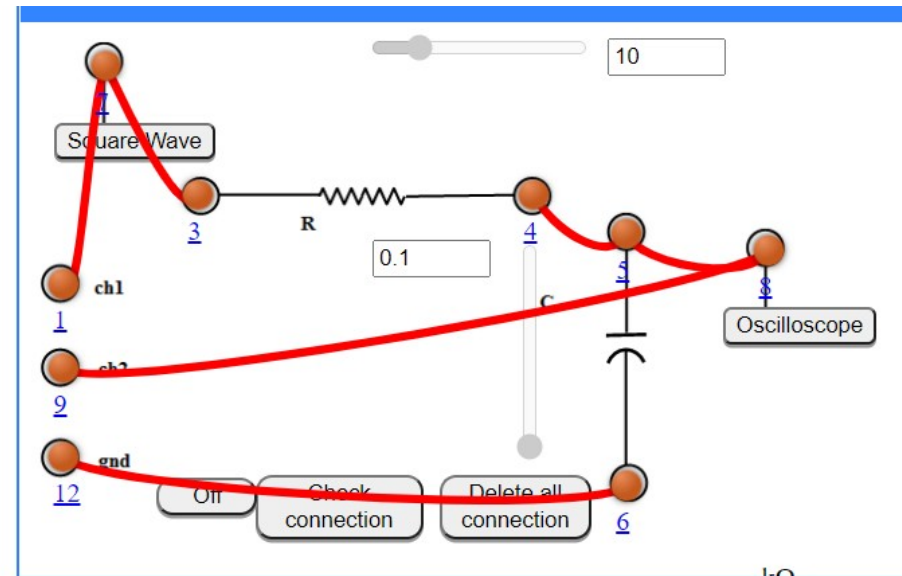


## CONTROLS

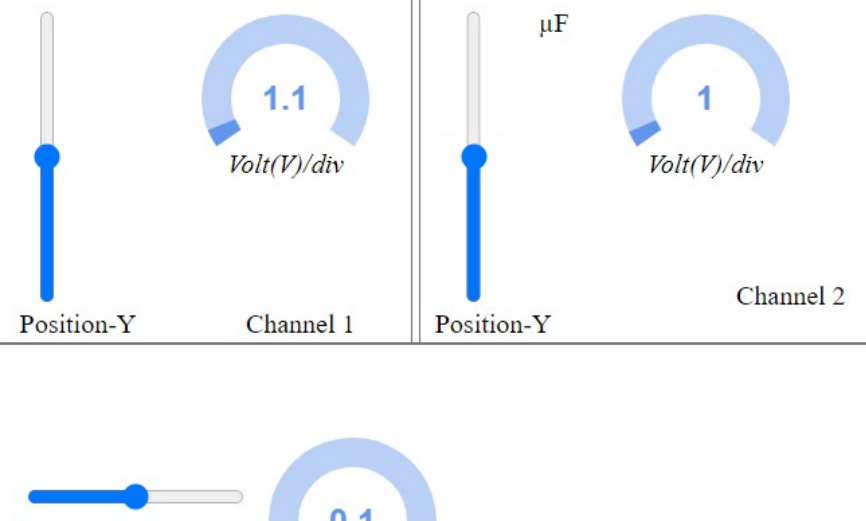



# Oscilloscope simulations for RC integrator circuit

## OSCILLOSCOPE

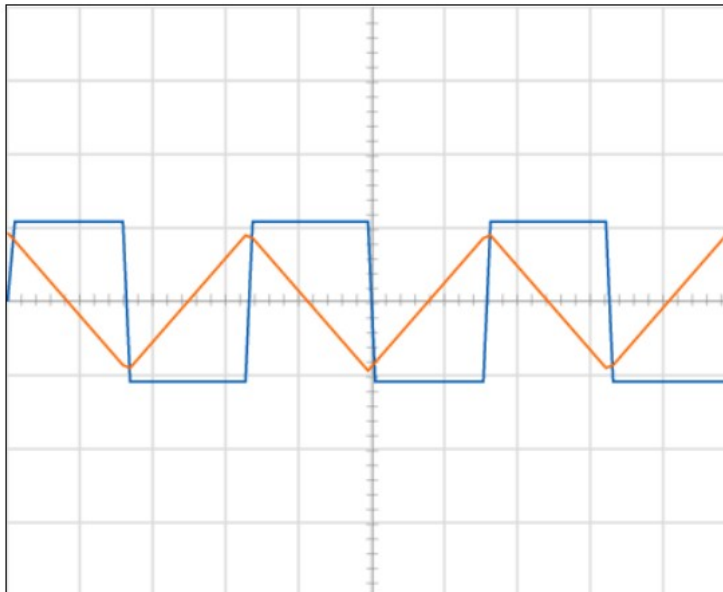

Channel 1


Channel 2

Ground


Dual

3000  
Frequency(Hz)

1.3  
Amplitude(Volt)

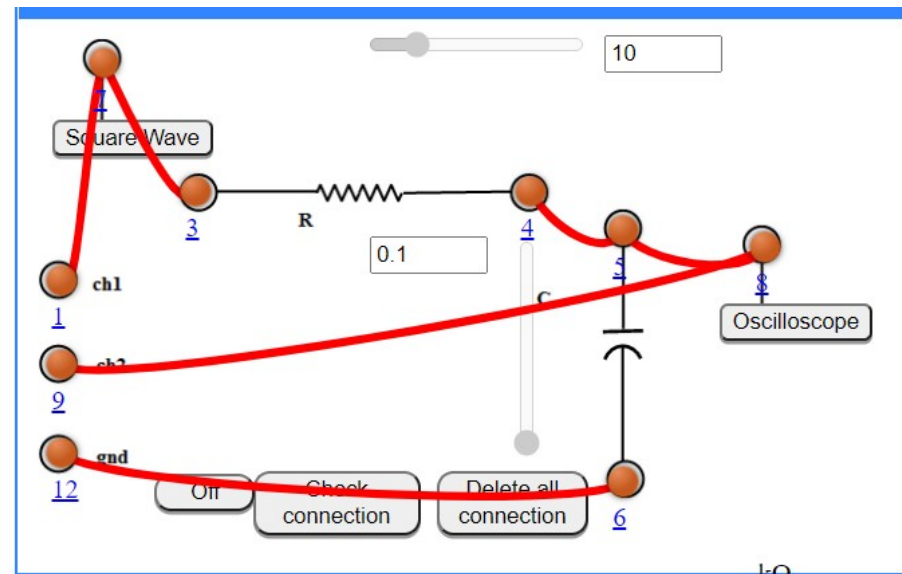

## CONTROLS

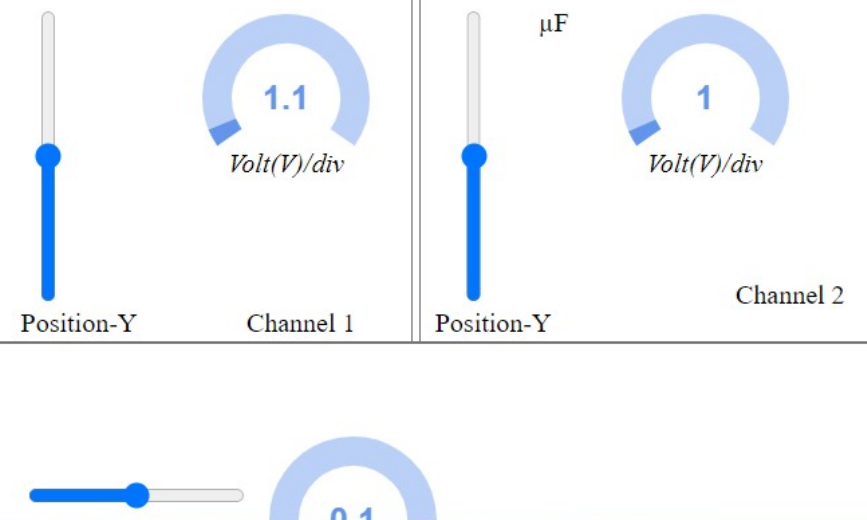



## Summary

- In this experiment, we learnt the principle behind charging and discharging of a RC Circuit.
- We also saw the construction and working of the RC Differentiator circuits which differentiates a square wave and converts into spikes.
- Next, we saw the construction and working of the RC Integrator which integrates the square wave to a triangular waveform.

## Observations

1. The frequency of output signal was not changing according to input frequency in RC differentiator circuit. (A glitch in vlab)
2. The square wave input is not ideal in practical experiment.